

UNIT-2

NON-LINEAR WAVE SHAPING

Non-Linear Wave Shaping

Definition: The process where by the form of a signal is changed by transmission through a non-linear network is called **Non-linear Wave Shaping**.

Types:

- i. Clippers.
- ii. Clampers.

Clipper Classifications

According to biasing, the clippers may be classified as

- Unbiased clippers and
- Biased clippers.

According to configuration used the clippers may be

- Series diode clippers
- Parallel or shunt diode clippers
- A series combination of diode, resistor and reference supply
- Multi-diode clippers consisting of several diodes, resistors and reference voltages
- Two emitter-coupled transistors operating as an over-driven

Contd...



According to level of clipping the clippers may be

- Positive clippers
- Negative clippers
- Biased clippers and
- Combination clippers

Clipper

- Clipping circuits are used to remove the part of a signal that is above or below some defined reference level.
- Clippers also known as
Voltage limiters
Current limiters
Amplitude selectors
Slicers


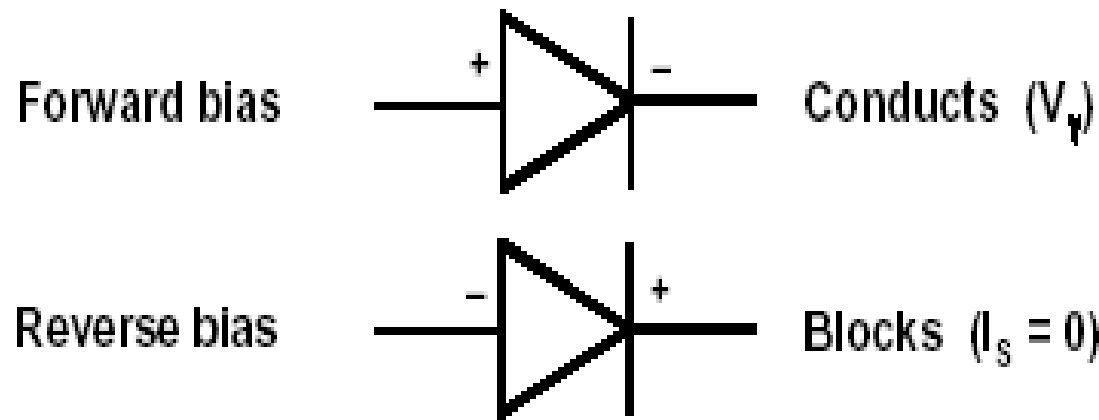
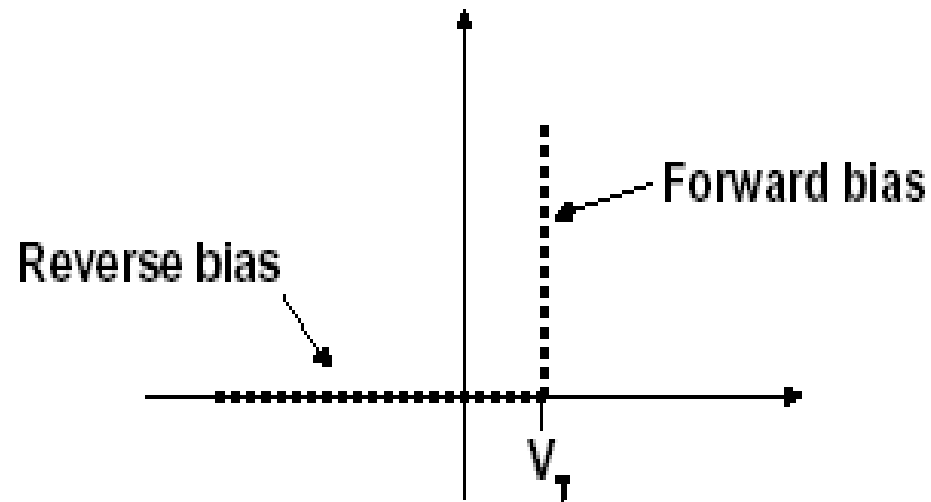
Let's again consider piecewise linear diode model



Unbiased clippers(Parallel Positive Clippers)

- **Without** the battery, the output of the circuit below would be the negative portion of the input wave (assuming the bottom node is grounded). When $v_i > 0$, the diode is on (short-circuited), v_i is dropped across R and $v_o = 0$. When $v_i < 0$, the diode is off (open-circuited), the voltage across R is zero and $v_o = v_i$.



Input signal, $v_i(t)$

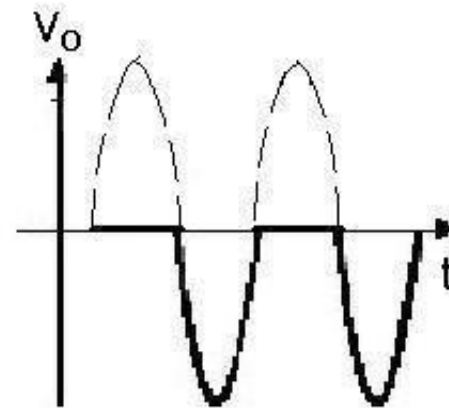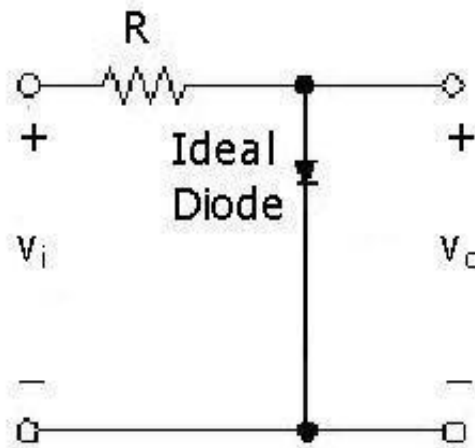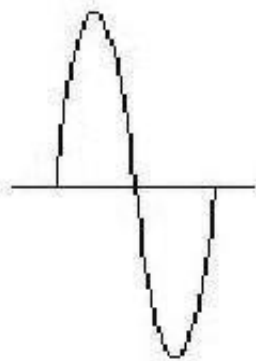


Unbiased clippers(Parallel Negative Clippers)

+ive cycle :- anode is at ground potential and cathode sees variable +ive voltage from 0 to $+V_m$. So complete cycle, the diode is reverse biased and $V_o = V_{in}$. At positive peak $V_o = +5V$

-ive cycle :- anode is at ground potential and cathode sees variable -ive volts from 0 to $-V_m$. When magnitude of input voltage i.e. $|V_{in}| > V_d$, the diode becomes forward biased and hence $V_o = -V_d = 0.7V$

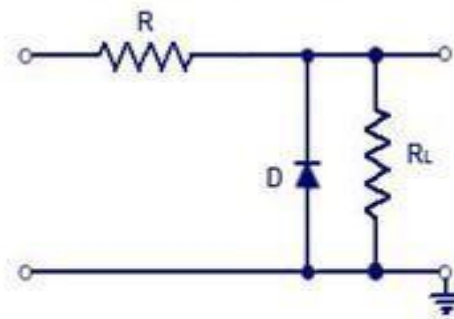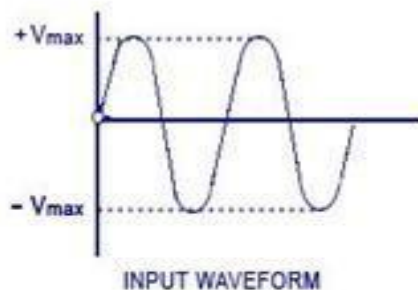

(b) Negative Shunt Clipper

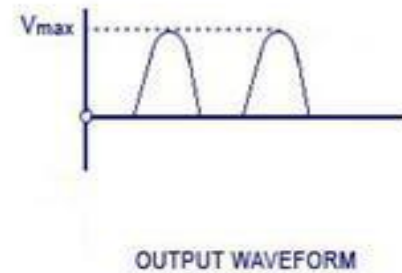


Series positive clipper

+ive cycle :- anode is at ground potential and cathode sees variable +ive voltage from 0 to $+V_m$. For complete cycle, diode becomes reverse biased and hence $V_o = 0V$


-ive cycle :- anode is at ground potential and cathode sees variable -ive voltage from 0 to $-V_m$. So in complete cycle, the diode is forward biased and $V_o = V_{in} + V_d$ and At negative peak,

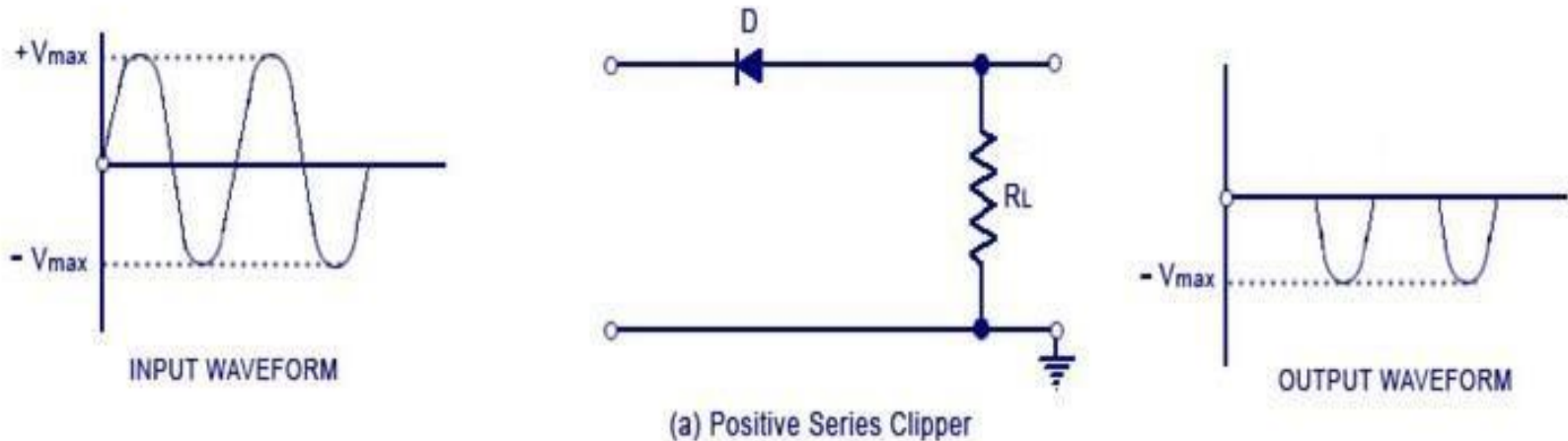Positive Series Clipper and Positive Shunt Clipper





Series Negative clipper

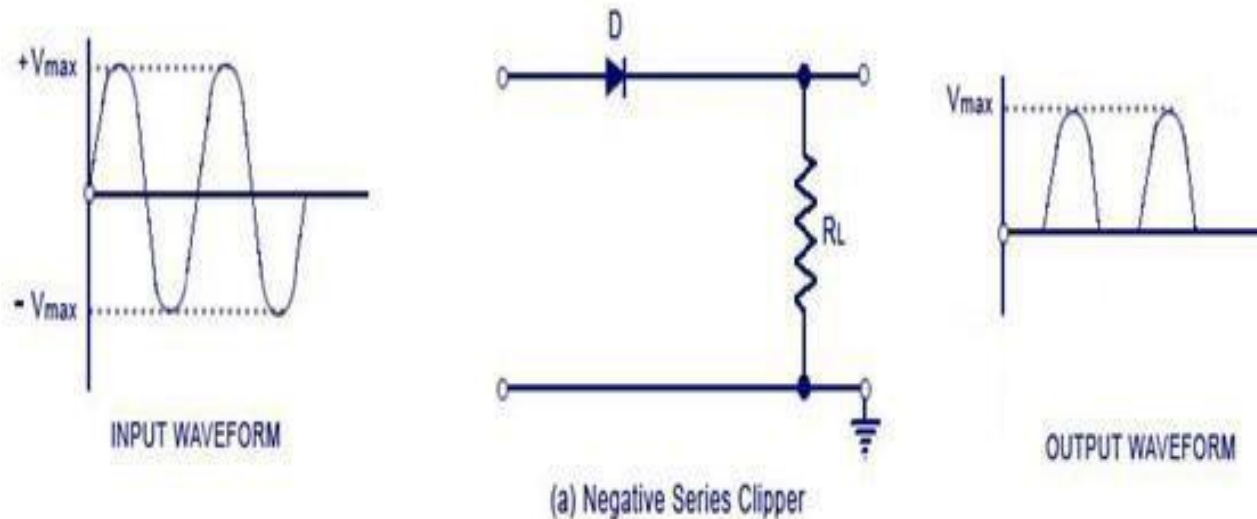
- +ive cycle :-** anode is at positive potential from 0 to $+V_m$. For complete cycle, diode becomes forward biased and hence $v_o = V_m$
- ive cycle :-** Cathode is at ground potential and cathode sees variable negative voltage from 0 to $-V_m$. So in complete cycle, the diode is Reverse biased and negative peak, $v_o = 0$



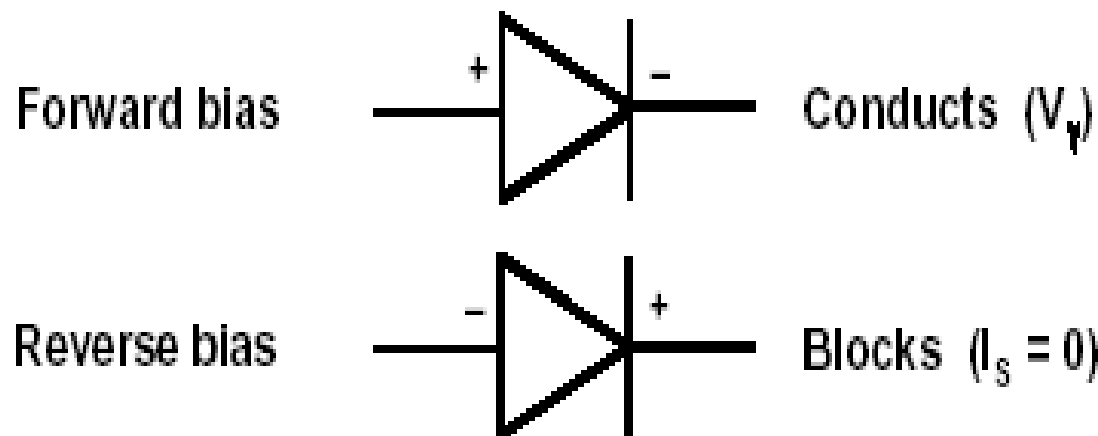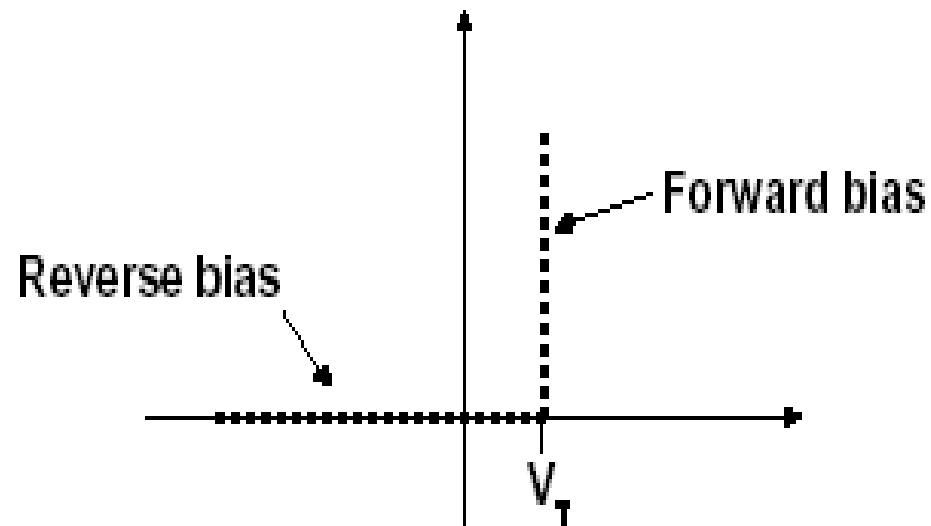Let's again consider piecewise linear diode model



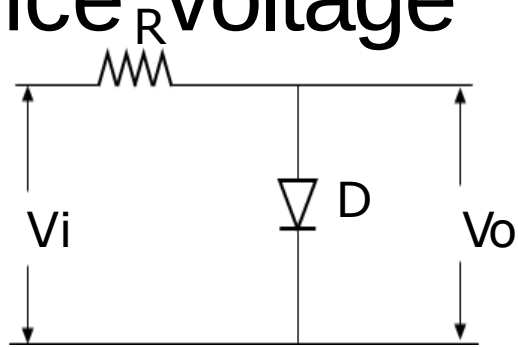
Positive Shunt clipping with zero reference voltage




Transfer characteristics equations:

$$\left. \begin{array}{l} V_o = 0 \text{ for } V_i > 0 \\ V_o = V_i \text{ for } V_i < 0 \end{array} \right\} \text{ [Ideal]}$$
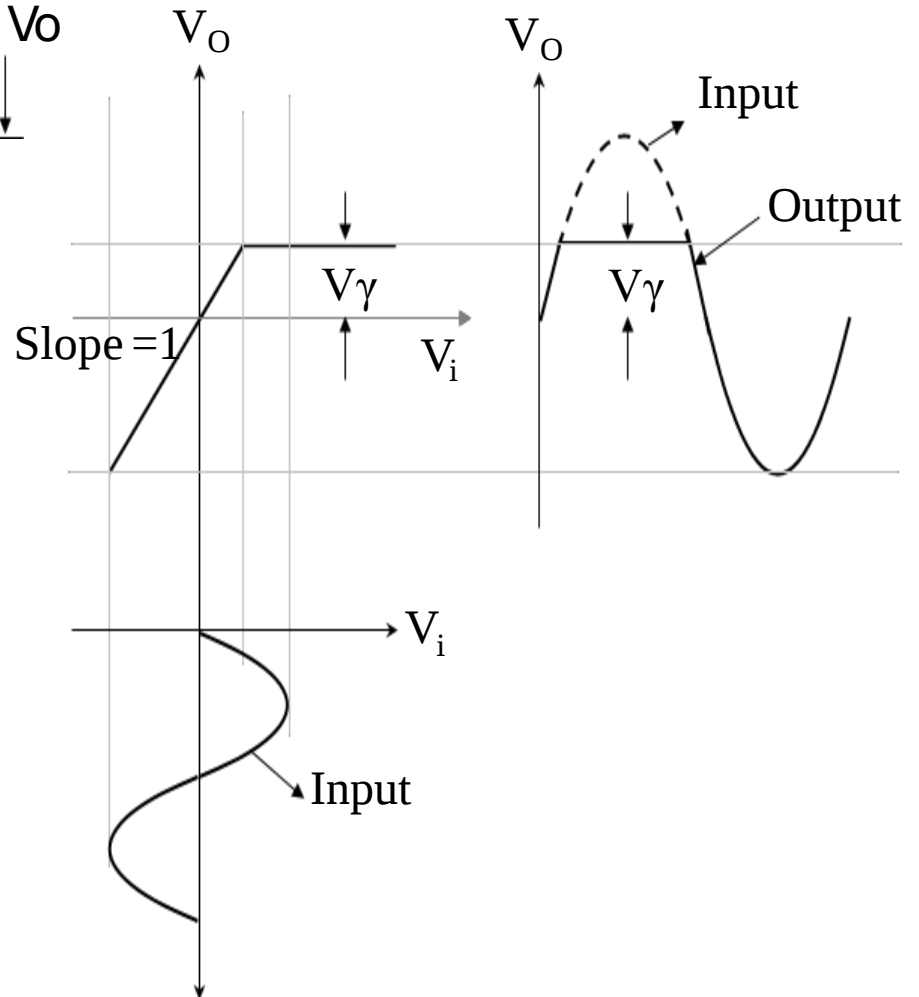
$$\begin{array}{ll} V_o = V_\gamma \text{ for } V_i > V_\gamma & \text{D - ON} \\ V_o = V_i \text{ for } V_i < V_\gamma & \text{D - OFF} \end{array}$$



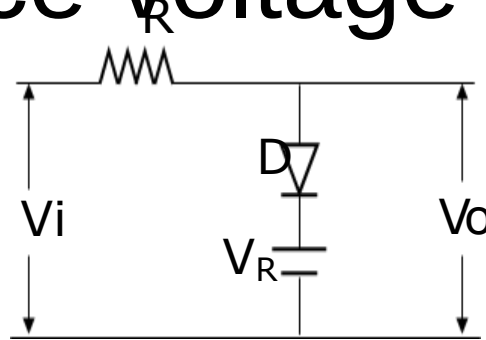Positive Shunt clipping with positive reference voltage




Transfer characteristics equations:

$$V_i < V_R + V_\gamma \quad D - \text{OFF}$$


$$V_O = V_i$$

$$V_i > V_R + V_\gamma \quad D - \text{ON}$$

$$V_O = V_R + V_\gamma$$

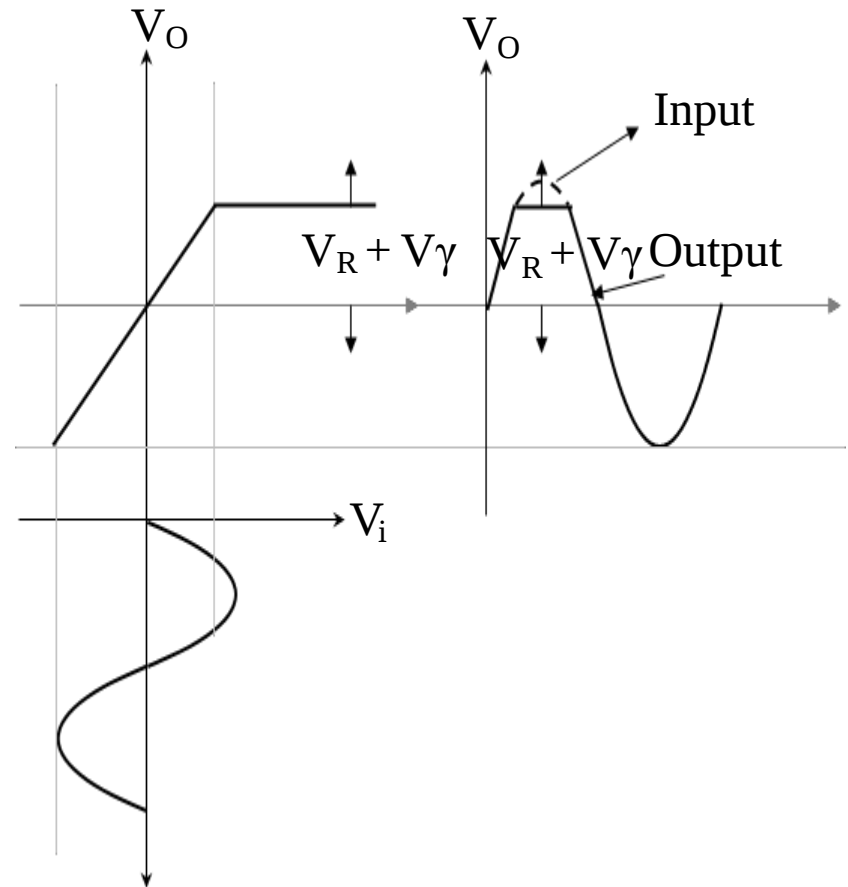

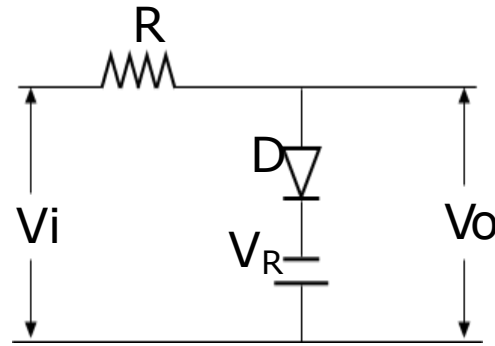Positive Shunt clipping with negative reference voltage




Transfer characteristics equation:

$$V_i > V_\gamma - V_R \quad D - \text{ON} \quad V_o$$


$$= V_\gamma - V_R$$

$$V_i < V_\gamma - V_R \quad D - \text{OFF}$$

$$V_o = V_i$$

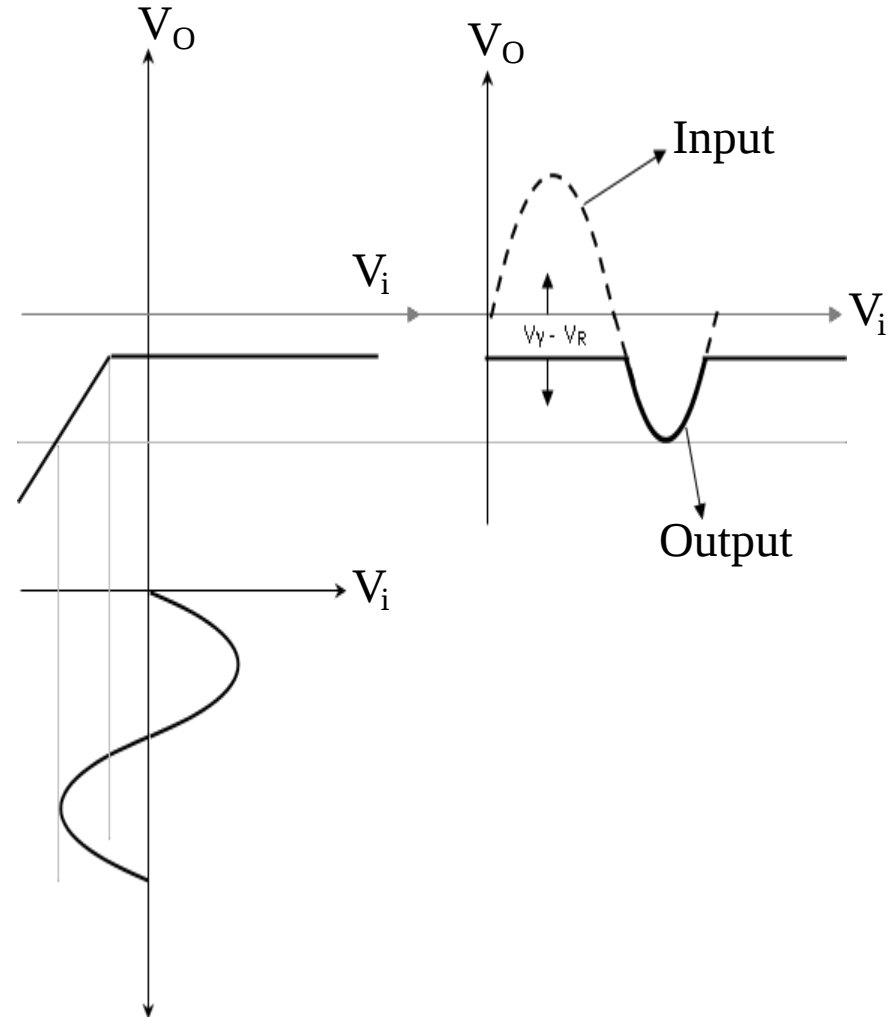

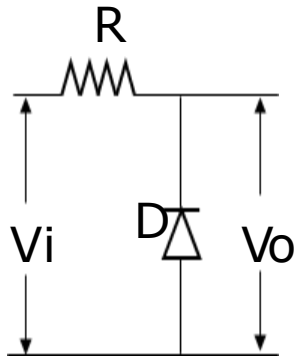
Negative Shunt clipping with zero reference voltage




Transfer characteristic equations:

$$V_i > -V_\gamma \quad D - \text{OFF} \quad V_o = V_i$$
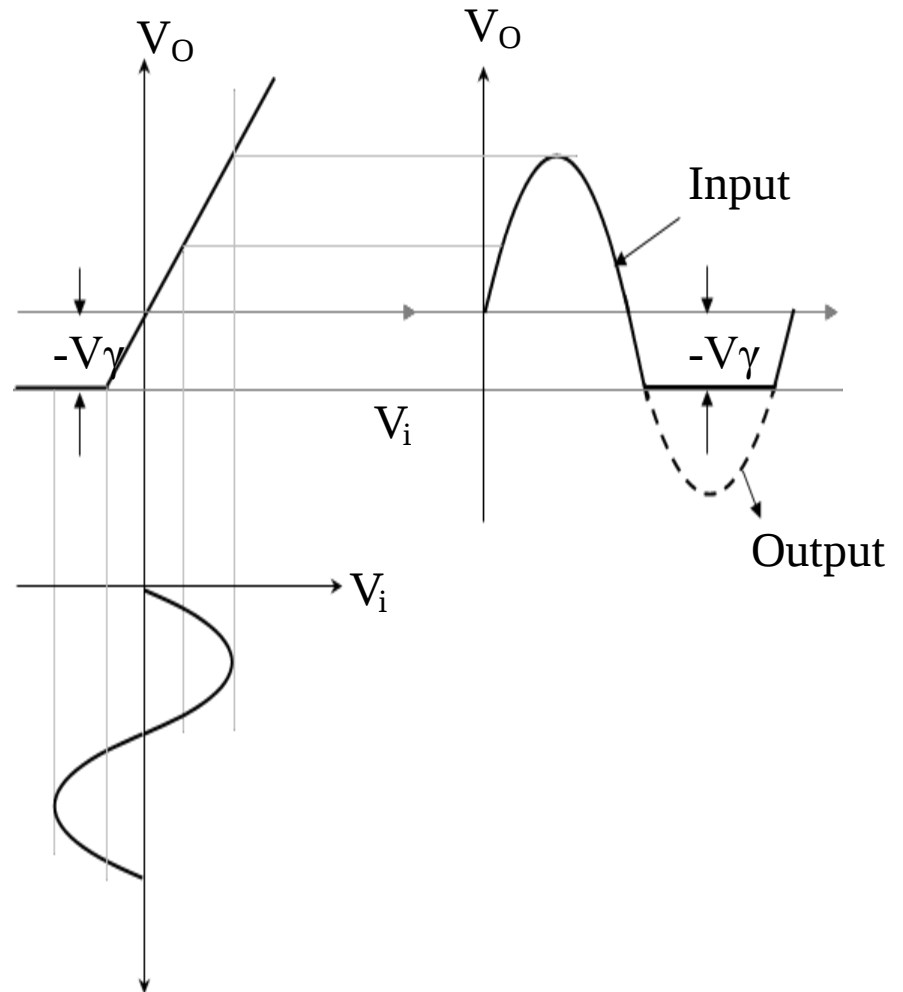
$$V_i < -V_\gamma \quad D - \text{ON} \quad V_o = -V_\gamma$$



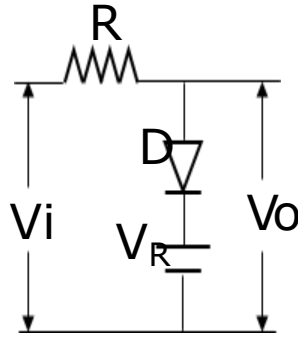Negative Shunt clipping with positive reference voltage




Transfer characteristics
equations:

$$V_i < V_R - V_\gamma \quad D - \text{ON}$$


$$V_o = V_R - V_\gamma$$

$$V_i > V_R - V_\gamma \quad D - \text{OFF}$$

$$V_o = V_i$$

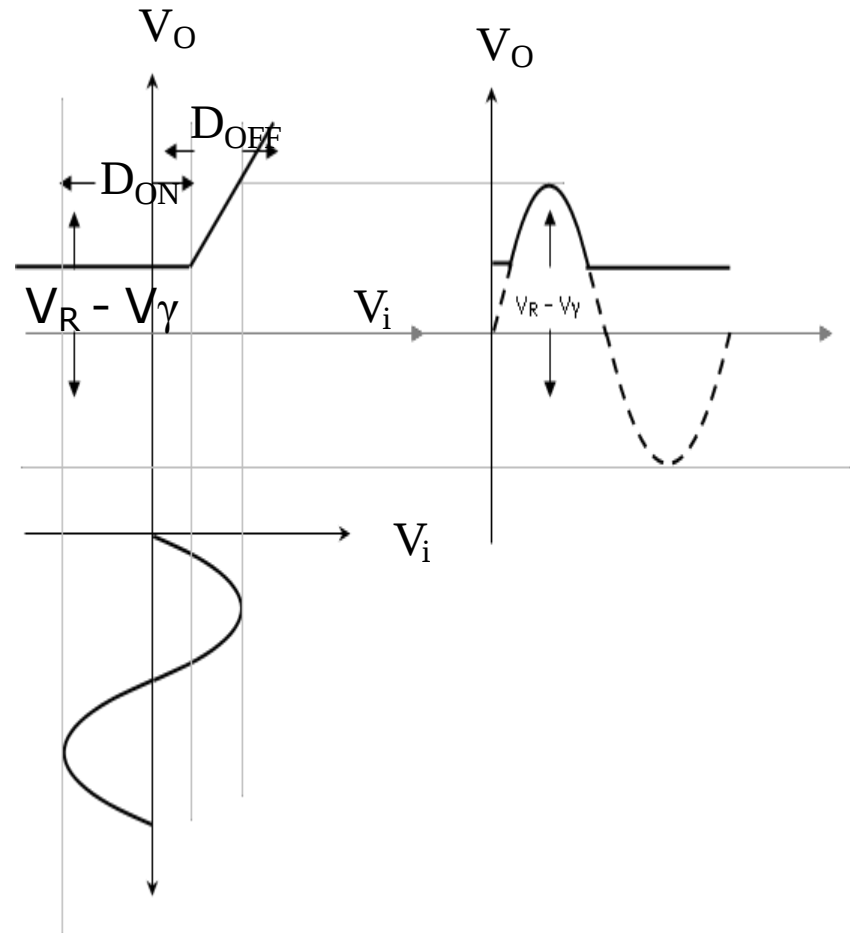

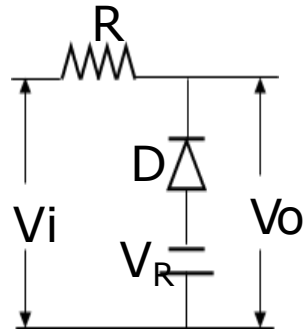
Negative Shunt clipping with negative reference voltage




Transfer characteristic equations:

$$\begin{aligned} V_i < -(V_\gamma + V_R) \quad D - \text{ON} \quad V_o \\ = -(V_\gamma + V_R) \end{aligned}$$
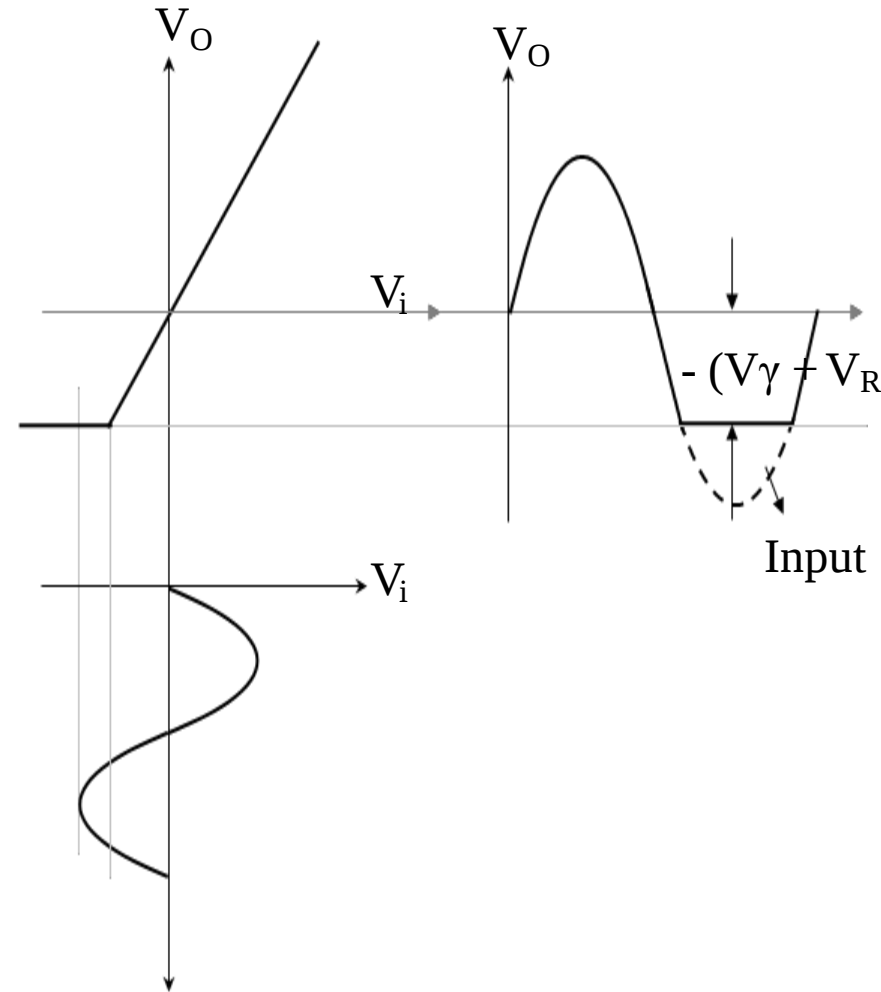
$$V_i > -(V_\gamma + V_R) \quad D - \text{OFF} \quad V_o = V_i$$



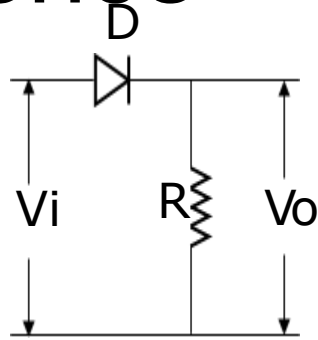
Negative Series clipper with zero reference




Transfer characteristic equations:

$V_i < 0$	D-OFF	$V_o = 0$	} Ideal Diode
$V_i > 0$	D-ON	$V_o = V_i$	

$V_i < V_\gamma$	D-OFF	$V_o = 0$	} Practical Diode
$V_i > V_\gamma$	D-ON	$V_o = V_i - V_\gamma$	

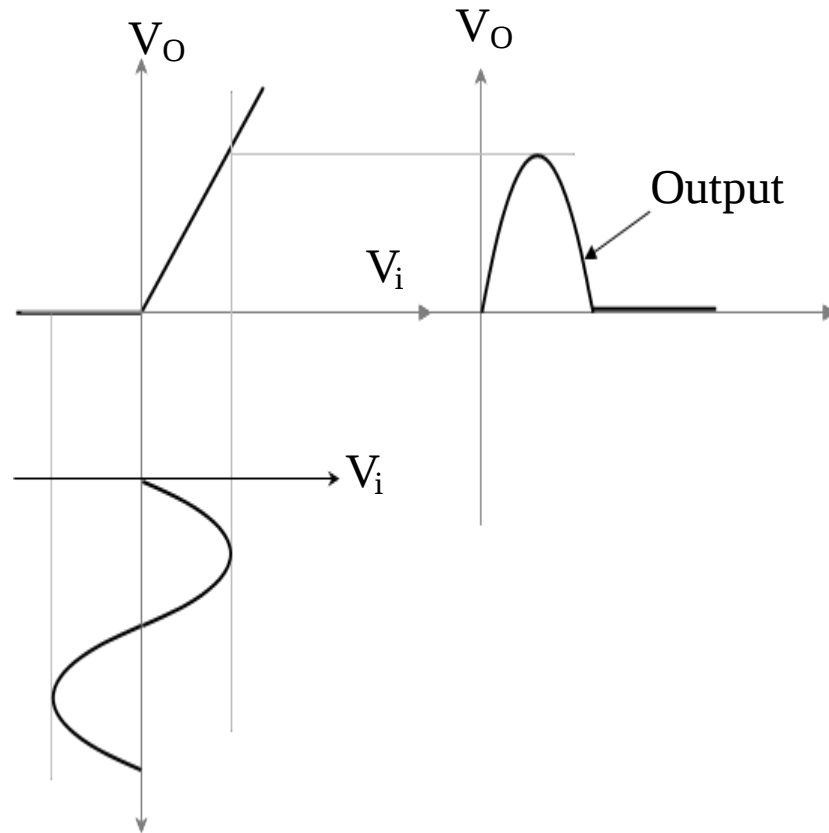


CLIPPING AT TWO INDEPENDENT LEVELS

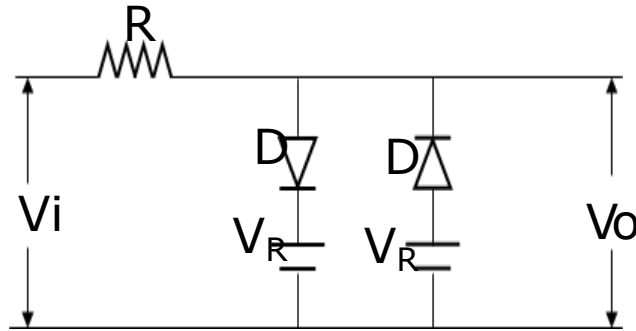



Transfer characteristic equations:

Input (V_i)	Diode State	Output (V_o)
$V_i \leq V_{R1}$	D_1 - ON, D_2 - OFF	$V_o = V_{R1}$
$V_{R1} < V_i < V_{R2}$	D_1 - OFF, D_2 - OFF	$V_o = V_i$
$V_i \geq V_{R2}$	D_1 - OFF, D_2 - ON	$V_o = V_{R2}$

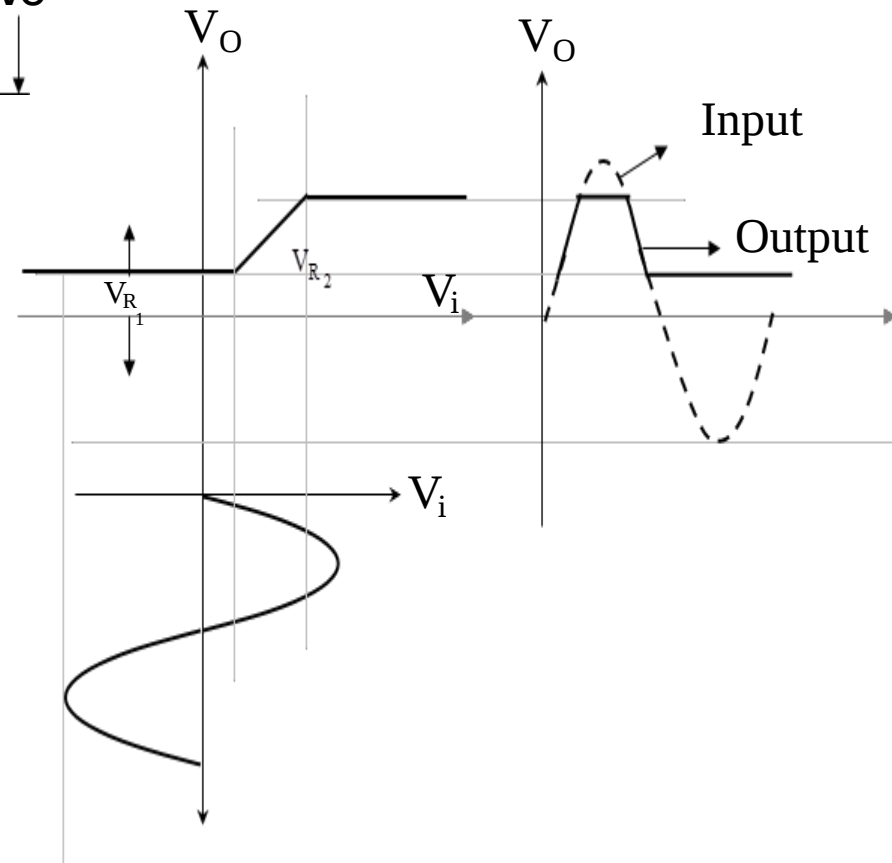

Contd..

TRANSISTOR CLIPPER WAVEFORMS

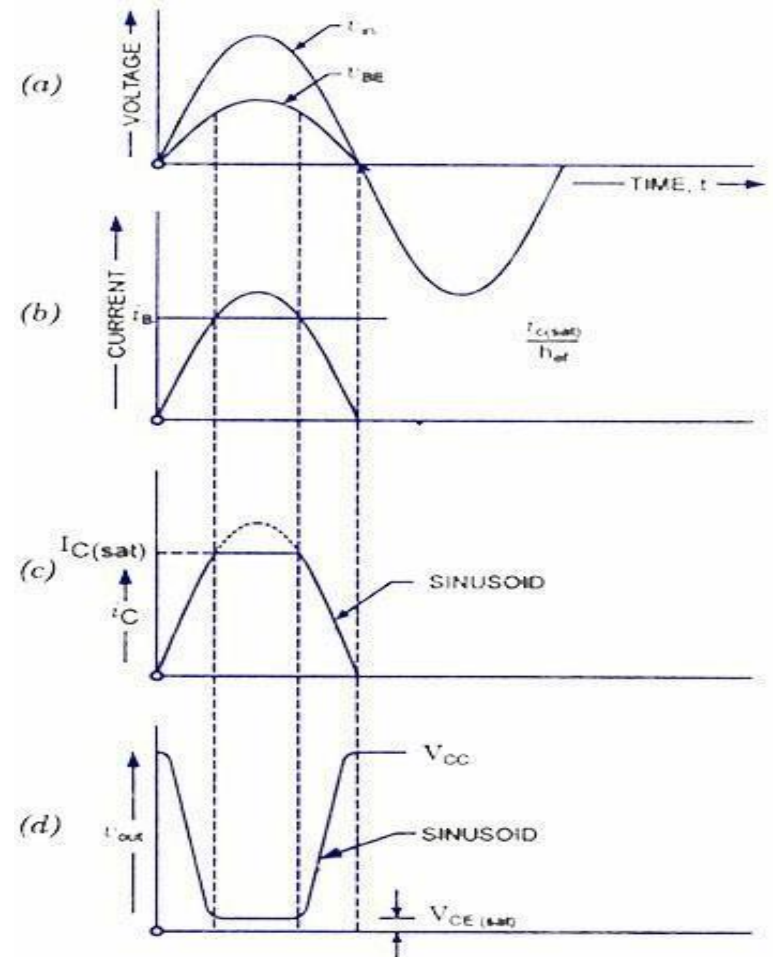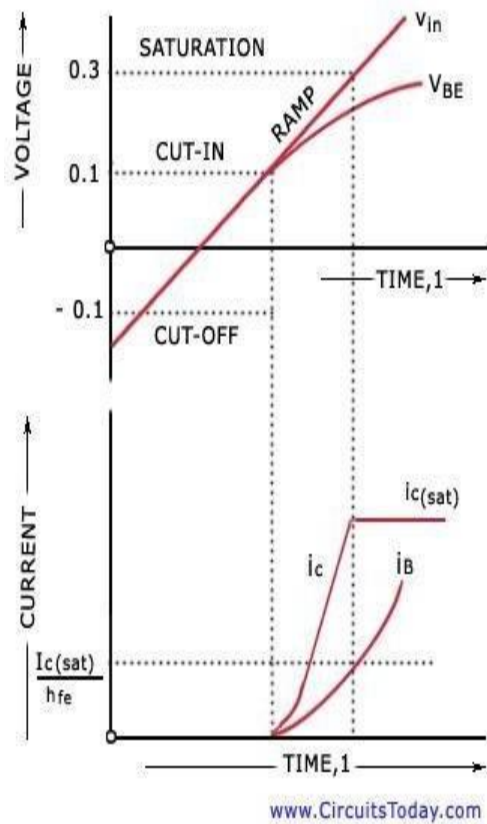


Transistor Clipper Waveforms For Sinusoidal Input

Transistor Clipper circuit

- The transistor has two types of linearities
 - One linearity happens when the transistor passes from cut-in region to the active region. The other linearity occurs when the transistor passes from the active region to the saturation region. When any input signal passes through the transistor, across the boundary between cut-in region and active region, or across the boundary between the active region and saturation region, a portion of the input signal

TRANSISTOR CLIPPER CIRCUIT

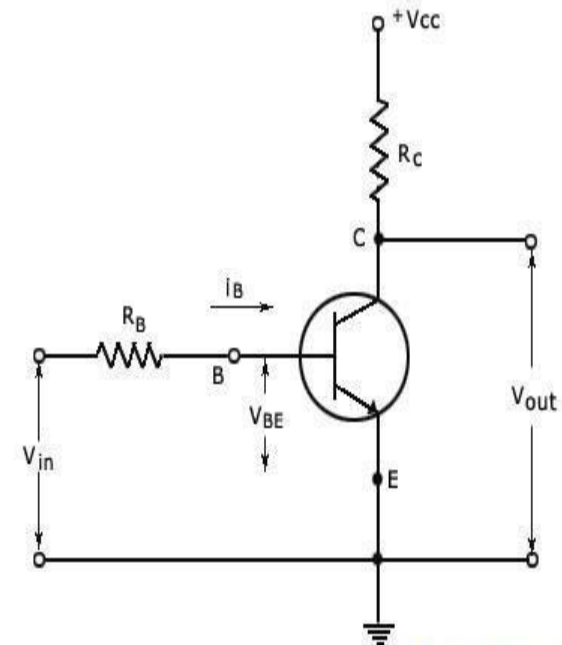

CLAMPING CIRCUIT

- The need to establish the extremity of the positive (or) negative signal excursion at some reference level. When the signal is passed through a capacitive coupling network such a signal has lost its d.c. component. The clamping circuit introduces the d.c. components at the outside, for this reason the coupling circuits are referred to as d.c. restore (or) d.c. reinserter.
- Def : “ A clamping circuit is one that takes an input waveform and provides an output i.e., a faithful replica of its shape, but has one edge clamped to the zero voltage reference point.


There are two types of clamping circuits.

- 1) Negative clamping circuit.
- 2) Positive clamping circuit.



Diode :- Clamper

Positive Clamper

The circuit for a positive clamper is shown in the figure. During the negative half cycle of the input signal, the diode conducts and acts like a short circuit. The output voltage $V_o \Rightarrow 0$ volts. The capacitor is charged to the peak value of input voltage V_m . and it behaves like a battery. During the positive half of the input signal, the diode does not conduct and acts as an open circuit. Hence the output voltage $V_o \Rightarrow V_m + V_m$. This gives a positively clamped voltage.

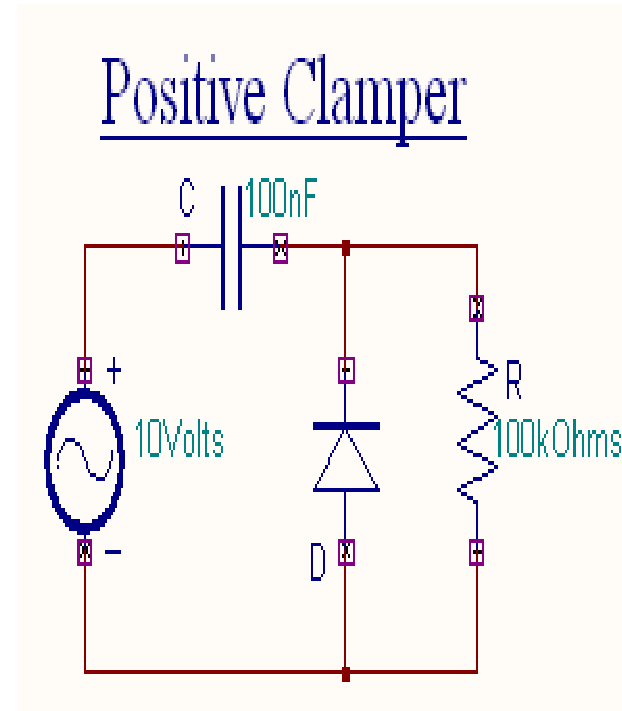


$$V_o \Rightarrow V_m + V_m = 2V_m$$

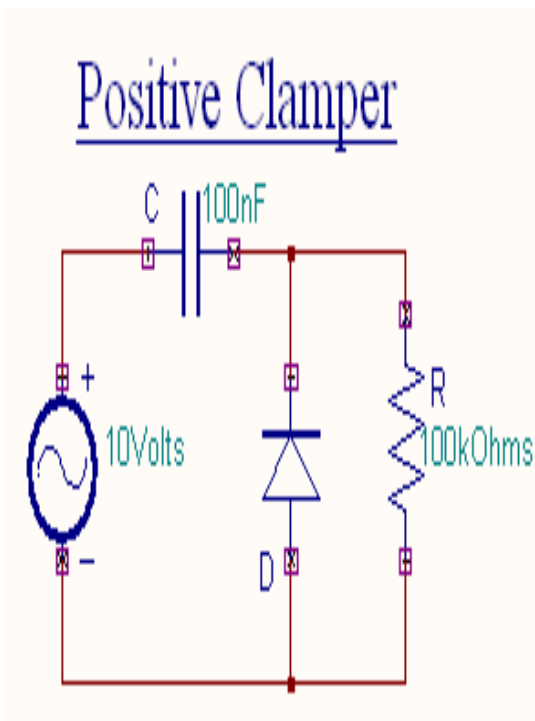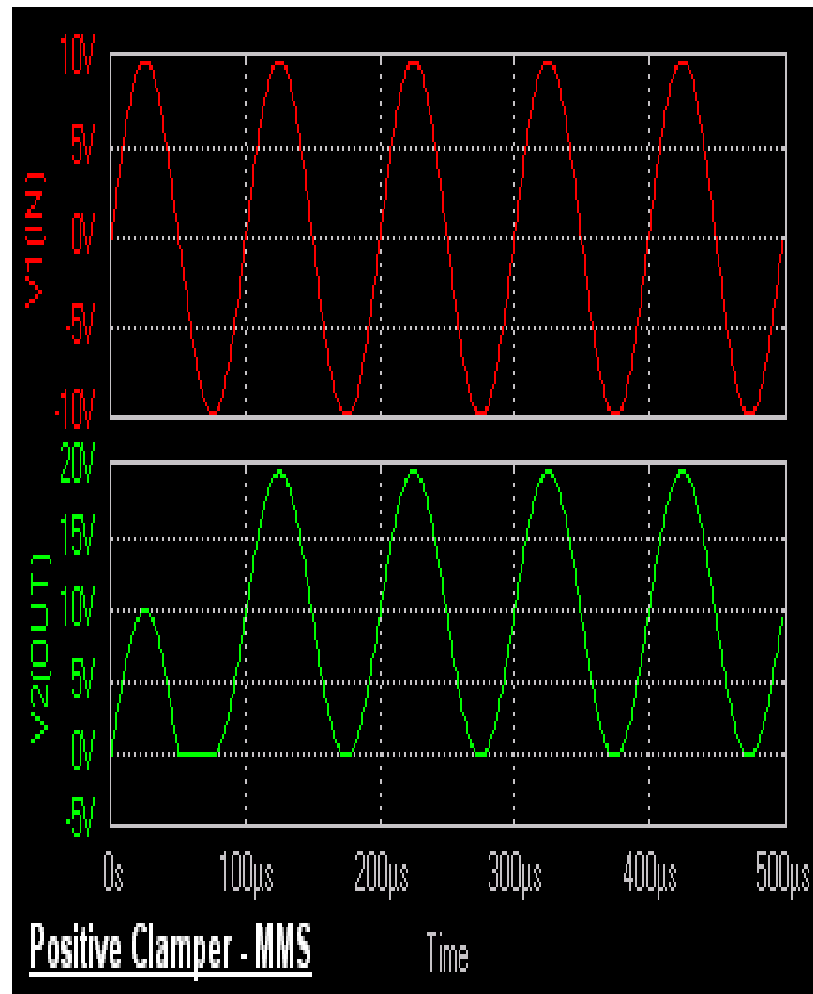


Negative Clamper

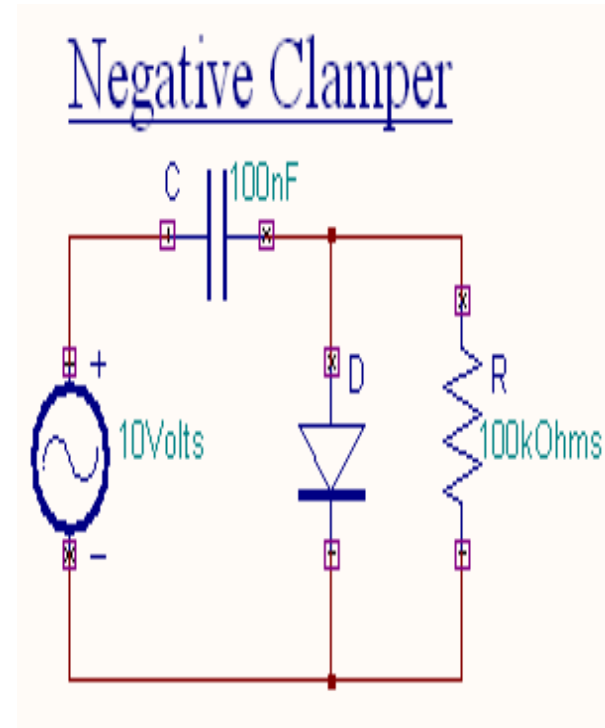
During the positive half cycle the diode conducts and acts like a short circuit. The capacitor charges to peak value of input voltage V_m . During this interval the output V_o which is taken across the short circuit will be zero. During the negative half cycle, the diode is open. The output voltage can be found by applying KVL.



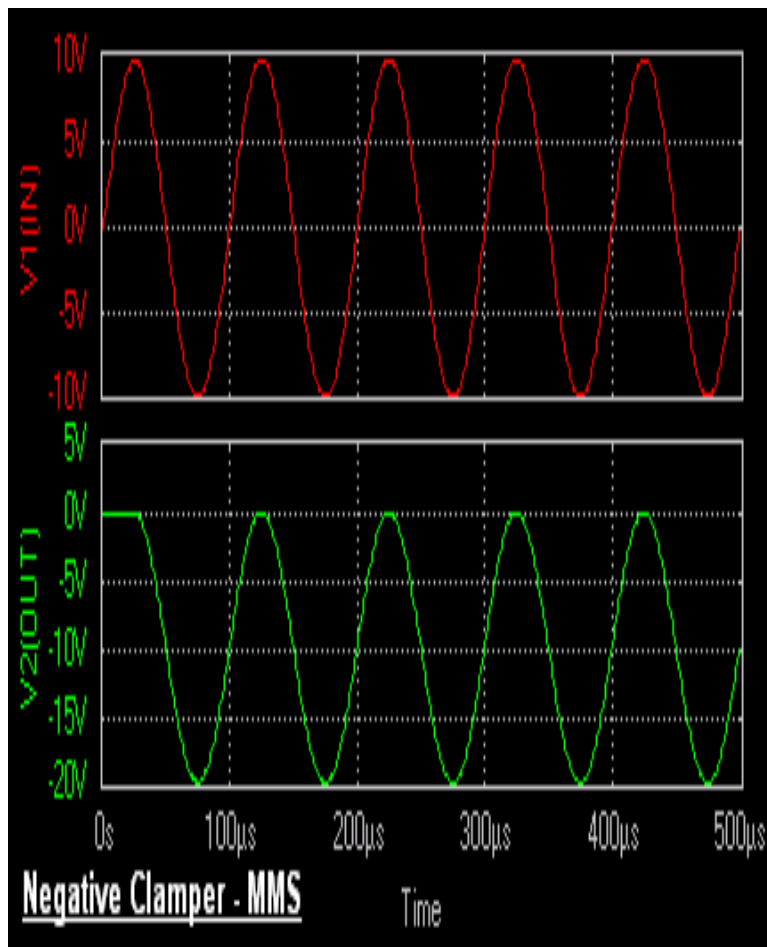
$$-V_m - V_m - V_o = 0 \quad V_o = -2V_m$$




Negative Clamper

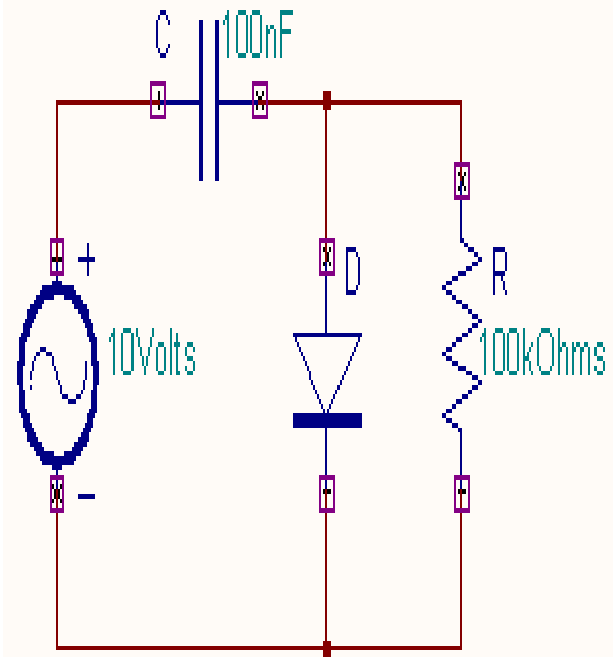

Biased Clamper

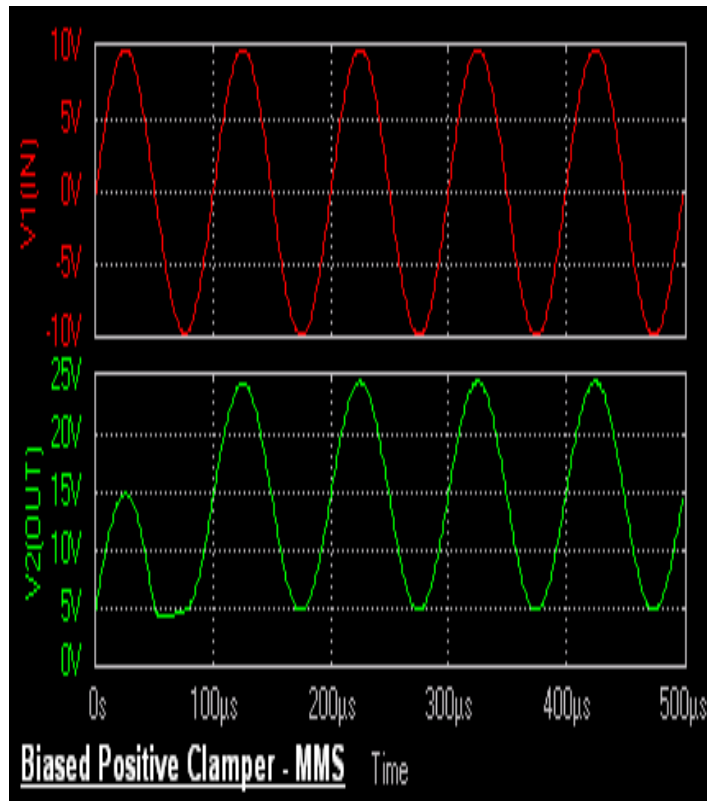

Biased Positive Clamper

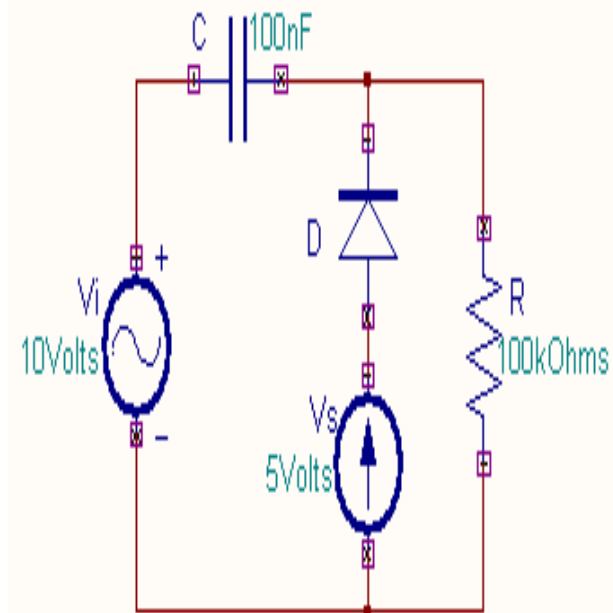

CLAMPING CIRCUIT THEOREM

- Therefore the charge acquired by the capacitor during the forward interval

$$\therefore \frac{A_f}{A_r} = \frac{R_f}{R}$$

Consider a square wave input is applied to a clamping circuit under steady state condition

If $V_f(t)$ is the output waveform in the forward direction, then from below figure the capacitor charging current is

$$i_f = \frac{V_f}{R_f}$$

Therefore the charge acquired by the capacitor during the forward interval

$$\int_0^{T_1} i_f dt = \frac{1}{R_f} \int_0^{T_1} V_f dt = \frac{A_f}{R_f} \dots\dots\dots (1)$$

• Similarly if $V_f(t)$ is the output voltage in the reverse direction, then the current which discharges by the capacitor is




$$i_r = \frac{V_r}{R}$$

$$\int_{T_1}^{T_2} i_r dt = \frac{1}{R} \int_{T_1}^{T_2} V_r dt = \frac{A_r}{R} \dots\dots\dots (2)$$



In the steady-state the net charge acquired by the capacitor must be zero.

Therefore from equation (1) & (2) this equation says that for any input waveform the ratio of the area under the output voltage curve in the forward direction to the reverse direction is equal to the ratio $\frac{R_f}{R_r}$.

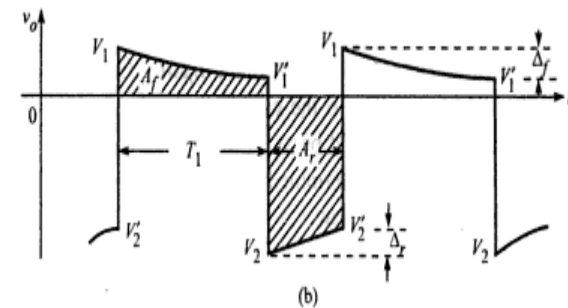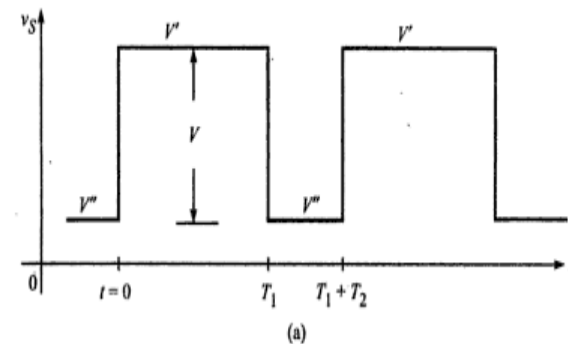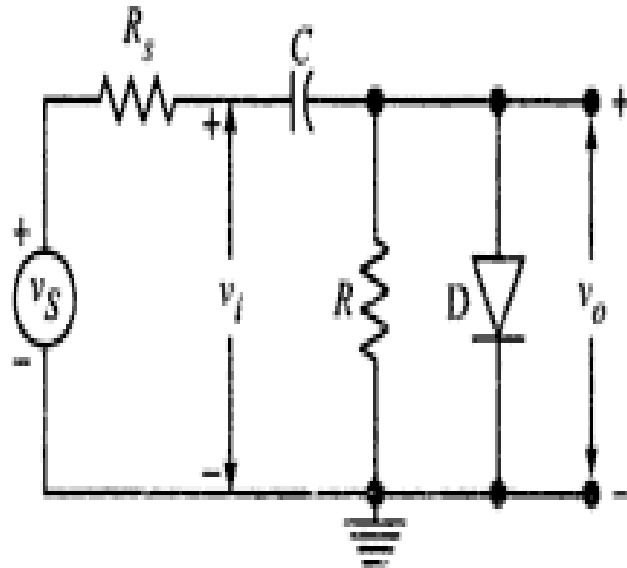
Clamping Circuit taking Source and Diode Resistances into account




Practical Clamping circuit

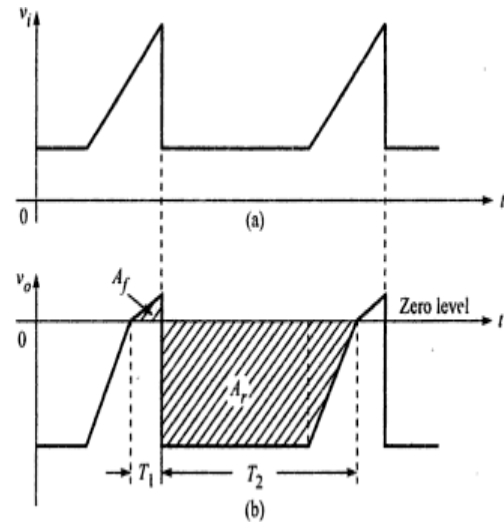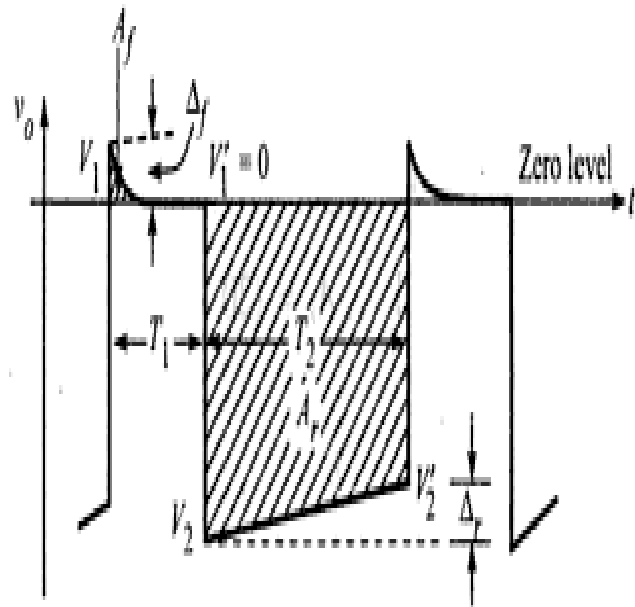

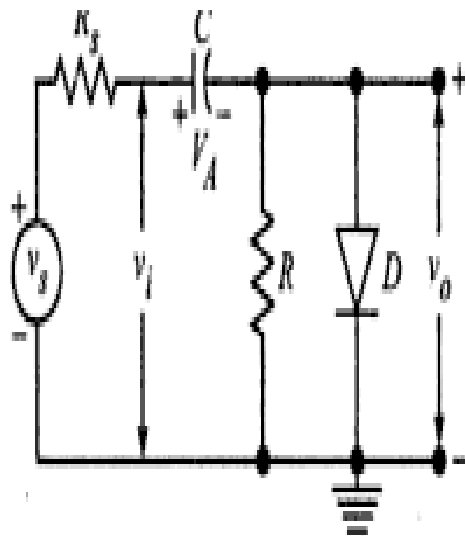Effect of diode characteristics on clamping voltage



(a)

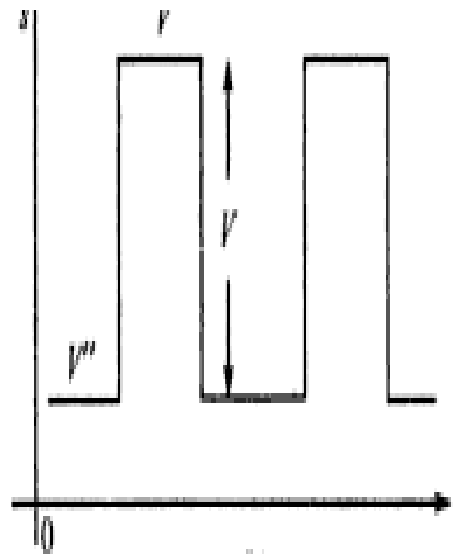

(b)

$$dV_{cl} = \eta V_T \frac{dV}{V}$$

Synchronized Clamping

