



ADITYA ENGINEERING COLLEGE (A)

VLSI Design-Unit IV

Basic Circuit Design Concepts & Scaling of MOS Circuits

P. Bujjibabu

Assistant Professor

Department of Electronics and Communication Engineering

Aditya Engineering College (A)

Email: bujjibabu_penumutchi@aec.edu.in



Course objectives

- COB 1: To enable the students learn various fabrication steps of IC and MOS, Bi CMOS processes
- COB 2: To enable the students learn basic electrical properties of MOS Transistors in analysis of circuits.
- COB 3: To make the students to study MOS technology-specific stick and layout rules
- COB 4: To make students to familiar with different circuit related parameters**
- COB 5: To enable the students to highlight the architecture design issues in the context of IC design



Course outcomes

At the end of the Course, Student will be able to:

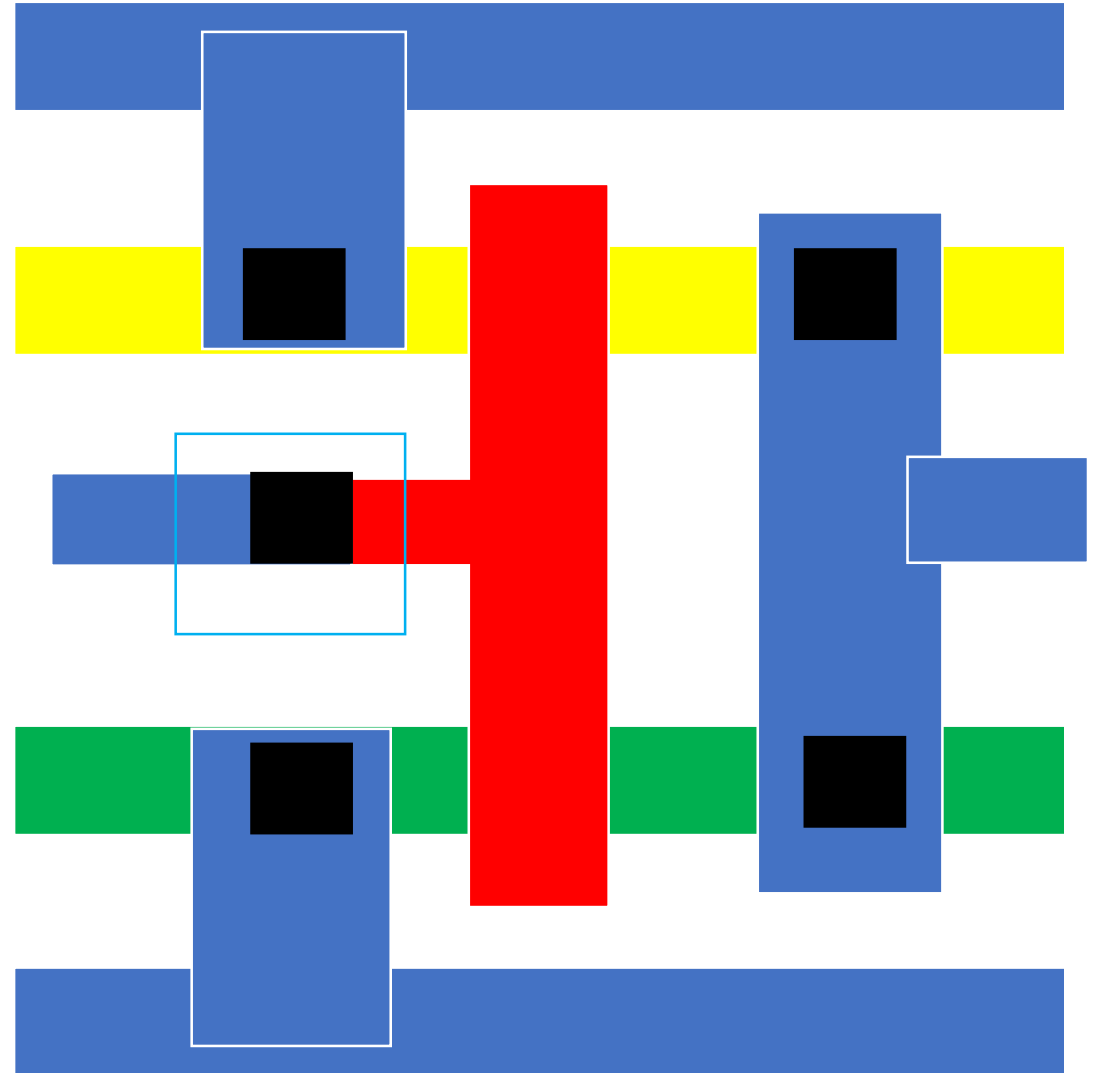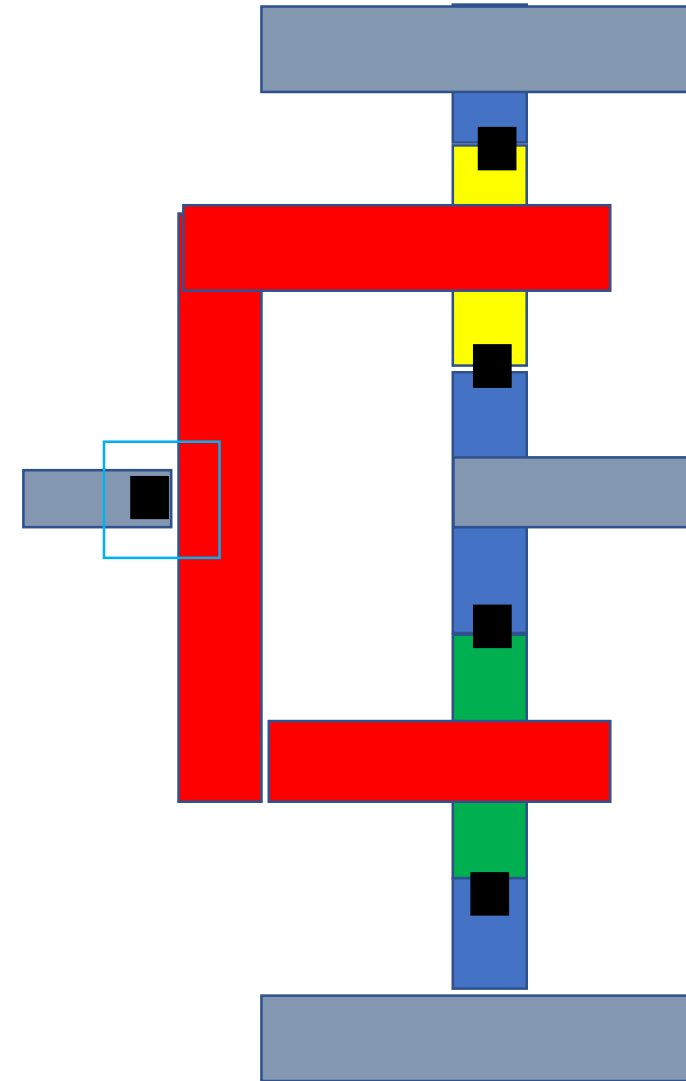- CO1: Outline the fundamental concepts related to MOS and Bi-CMOS Circuits fabrication.
- CO2: Analyze the electrical properties of MOS and Bi-CMOS Circuits.
- CO3: Make use of design rules for stick and layout diagrams.
- CO4: Infer the circuit parameters in modeling the logic/subsystem performance.**
- CO5: Interpret FPGA and ASIC design approaches for semi custom design



 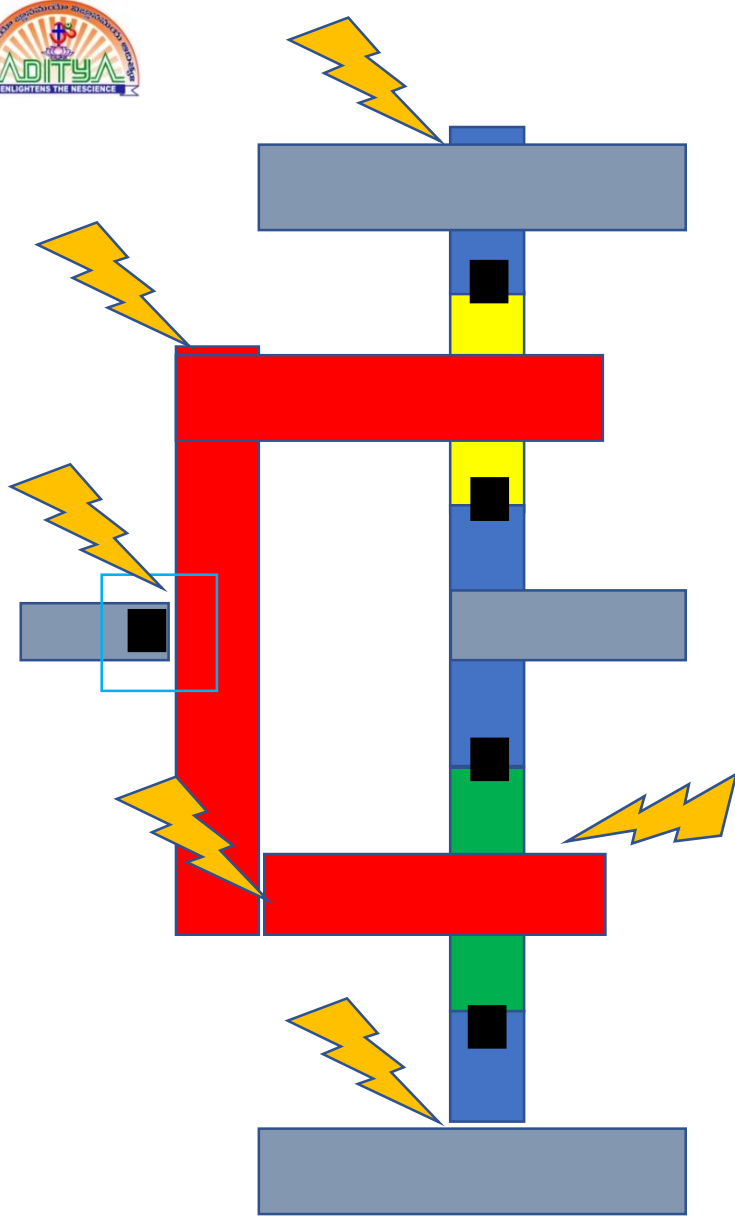Identify the points where there is possibility for DRC violations




Solution

- Minimum feature size
- Minimum distance or spacing
- Minimum overlap or extension





From Circuit to Chip

- Circuit design
- Layout with design rules (CAD system)
- Merge with test structures, merge to reticle
- Design rule check with program
- Generation of mask data
- Mask Fabrication: glass and chrome
- Step and repeat:
- Projection of mask onto photo resist on the chip

Over etch, smaller lines causing opens

 


$$V_{out} = V_{in}'$$

 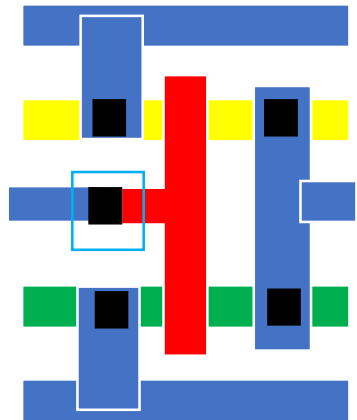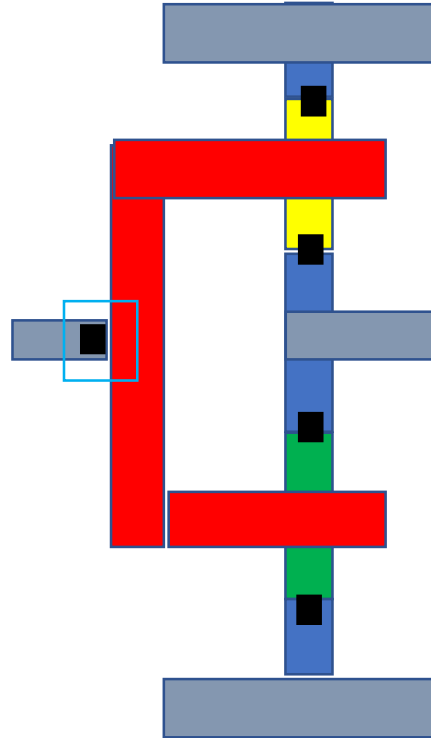 

- Define the statement from the problem.
- Draw the truth table
- Write Boolean expression for the outputs.
- **Simplify** the Boolean expressions
- **Draw the RTL (gates) diagrams**
- **Write HDL codes**(in different styles)
- Verify the synthesis report
- **Draw** the schematics(in different types)
- Simulate and check (power & delay)
- **Draw** the layout for the best schematic
- Physical verification(**PEX-parasitic's**)
- **Estimate C, R, Tr, Tf, Delays**

what is known as ckt. design concepts

 

Basic Circuit Design Concepts & Scaling of MOS Circuits

Basic Circuit Concepts:

- Sheet Resistance, and Sheet Resistance concept applied to MOS transistors and Inverters,
- Area Capacitance of Layers, Standard unit of capacitance,
- The Delay Unit, Inverter Delays, Propagation Delays,
- Wiring Capacitances.

Scaling of MOS Circuits:

- Scaling models, Scaling factors for device parameters,

Subsystem Design:

- Architectural issues, switch logic, Gate logic,
- Structured design, clocked sequential circuits,
- System considerations,
- The design process of the arithmetic processor.

Basic Circuit Concepts

• Introduction:

MOS Transistor is with **gate, source and drain forming regions** which consists of


S	←	▪ p+ or n+ diffusion
O	←	▪ polysilicon and
M	←	▪ metal layers

Separated
by insulating
layers

- Each layer has fundamental components like.,
 - Resistance ,Capacitance and Inductance

- Hence, the characterization and performance can be estimated by knowing .,

 - R,C, L, and associated Delays
- Power & Clock distribution through Tr size
- Power consumption& Charge Sharing Mechanism
- Effects of scaling and Reliability




1. Sheet Resistance,

- A uniform slab of semi-conducting material is shown in fig with the dimensions and the resistance of the slab is given by

$$R = \frac{\rho L}{A} = \frac{\rho}{t} \frac{L}{W} \quad \text{Which can be} \quad R = R_s \left(\frac{L}{W} \right)$$


- Where ρ is resistivity of the oxide layer
 - t; is the oxide thickness
 - L; is length oxide slab
 - W; is the width of slab
 - R_s is the sheet resistance in $\Omega/\square$
- Here the sheet resistance R_s depends on only resistivity and thickness of the oxide layer but not on length and width of the slab
- On resistance of a slab or MOSFET is given by $R_{on} = Z R_s$ with Z as aspect ratio of pull up or pull down device

 

Sheet Resistance and area dependence,

- The resistances of layers shown in below two figures are equal because of equal thickness and same value of resistivity

resistances of two layers ?

 


$$R_{\text{large}} = \frac{\rho}{t} \frac{2L}{2W} = \frac{\rho}{t} \frac{L}{W} = R_{\text{small}}$$

Rs concept applied to MOS transistors and Inverters

- Consider the two transistor layout structures as shown in below fig. with corresponding dimensions


$$R = \frac{\rho L}{A} = \frac{\rho}{t} \frac{L}{W}$$

Fig. a

 

$$R_a = \frac{\rho}{t} \frac{2\lambda}{2\lambda} = \frac{\rho}{t} \quad (1)$$


Fig. b

 

$$R_b = \frac{\rho}{t} \frac{8\lambda}{2\lambda} = \frac{\rho}{t} \quad (4)$$

Therefore, $R_b = 4 R_a$

 Rs concept applied to MOS transistors and Inverters



Hence, for an inverter $R_{on} = Z R_s$


$$R_{ontotal} = R_{onpu} + R_{onpd}$$

$$R_{ontotal} = Z_{pu} R_{sp} + Z_{pd} R_{sn}$$

 Problems

$$R = \frac{\rho L}{A} = \frac{\rho}{t} \frac{L}{W}$$


Calculate on resistance of the circuit shown in the figure 4 from V_{DD} to GND. If n- channel sheet resistance $R_{sn}=10^4 \Omega$ per square and P-channel sheet resistance $R_{sp} = 3.5 \times 10^4 \Omega$ per square. [16]



$$R = \frac{\rho L}{A} = \frac{\rho}{t} \frac{L}{W}$$

Ex 1:

 Calculate on resistance of the circuit shown from V_{DD} to Gnd if n-channel sheet resistance $R_{sn} = 10^4 \Omega/\square$ and p-channel sheet resistance $R_{sp} = 2.5 \times 10^4 \Omega/\square$.




$$R = \frac{\rho L}{A} = \frac{\rho}{t} \frac{L}{W}$$

Ex 2: Calculate on resistance of the circuit from V_{DD} to Gnd for $R_{on} = 10^4 \Omega$ and $R_{op} = 3.5 \times 10^4 \Omega$ with $Z_{pu} = \frac{4}{4}$ & $Z_{pd} = \frac{2}{2}$.

Sol

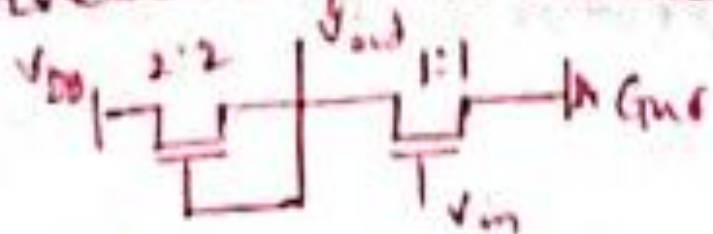Ex 3: Calculate on resistance from V_{DD} to ground for given inverter of n channel sheet resistance $R_{sh} = 2 \times 10^4 \Omega/\square$.



Ans = $40K\Omega/\square$.

2. Area Capacitance of Layers


- In a MOS, the conducting layers are separated by dielectric layers, which leads parallel plate capacitive effects.
- For any given layer, the area capacitance can be., $C = \frac{\epsilon A}{t_{ox}} = \frac{\epsilon_0 \epsilon_{ins} A}{t_{ox}}$ farads
- Where t_{ox} is thickness of layer(oxide) in cm
- A is area of plate in square cm
- ϵ_{ins} is relative permittivity of $SiO_2 = 4.0$
- ϵ_0 is absolute permittivity $8.854 \times 10^{-14} F / cm$
- The capacitance of a given area is calculated by taking the product of relative area of the layer and relative area capacitance. i.e.

$$C = \square C_g \times \left[\frac{\text{Area of layer given}}{\text{Area of standard square}} \right] = \square C_g \times \left[\frac{A}{A_{\square}} \right]$$

- Where $\square C_g$ is relative capacitance and is technology dependent [given in table]
- A is area of a given layer
- $A_{\square}$ is the area of a standard square in given feature unit(lambda or micron)

Standard unit of Capacitance,

- It is convenient to employ a **standard unit of capacitance** that can be given a value appropriate to technology but can also be used in calculations without associating it with an absolute value. **The standard unit of capacitance is defined as the gate-to-channel capacitance of a MOS transistor having $W=L$ i.e. a standard technology or a feature size as shown in fig, denoted by $\square C_g$**
- Here the gate capacitance $\square C_g$ is depending on W & L and may be evaluated for any MOS process

 

Ex 1: for a 5 um Technology MOS structure;

Area of a standard square is $5\mu\text{m} \times 5\mu\text{m} = 25 \mu\text{m}^2$

Capacitance = $4 \times 10^{-4} \text{ pF}/\mu\text{m}^2$

Thus the standard unit of capacitance

$$\square C_g = C_g \cdot A_{\square} = 4 \times 10^{-4} \text{ pF}/\mu\text{m}^2 \times 25 \mu\text{m}^2 = 0.01 \text{ pF}$$

Ex 2: for a 2 um Technology MOS structure;


Area of a standard square is $2\mu\text{m} \times 2\mu\text{m} = 4 \mu\text{m}^2$

Capacitance = $8 \times 10^{-4} \text{ pF}/\mu\text{m}^2$

Thus the standard unit of capacitance

$$\square C_g = C_g \cdot A_{\square} = 8 \times 10^{-4} \text{ pF}/\mu\text{m}^2 \times 4 \mu\text{m}^2 = 0.0032 \text{ pF}$$

Some area Capacitance calculations

 

Typical area capacitances in $10^{(-4)}$ pF

Layer name	Technology		
	5um	2um	1.2um
Gate-to-channel	4(1.0)	8(1.0)	16(1.0)
Diffusion (Active)	1(0.25)	1.75(0.22)	3.75(0.23)
Poly-to-substrate	0.4(0.1)	0.6(0.075)	0.6(0.038)
Metal1-to-substrate	0.3(0.075)	0.33(0.04)	0.33(0.02)
Metal2-to-substrate	0.2(0.05)	0.17(0.02)	0.17(0.01)
Metal2-to- Metal1	0.4(0.1)	0.5(0.06)	0.5(0.03)
Metal1-to-Poly	0.3(0.075)	0.3(0.038)	0.3(0.019)

Some area Capacitance calculations

Ex 1: for a 5 um Technology MOS structure;

Area of a standard square is $5\mu\text{m} \times 5\mu\text{m} = 25 \mu\text{m}^2$

Capacitance = $4 \times 10^{(-4)} \text{ pF}/\mu\text{m}^2$

Typical area capacitances in $10^{(-4)} \text{ pF}$

Thus the standard unit of capacitance

$$\square C_g = C_0 \cdot A_{\square} = 4 \times 10^{(-4)} \text{ pF}/\mu\text{m}^2 \times 25 \mu\text{m}^2 = 0.01 \text{ pF}$$

Some area Capacitance calculations

$$C = \epsilon C_g (A/A_\square)$$

Where; A is the area of given layer $= 3\lambda \times 20\lambda = 60\lambda^2$

$A_\square$ is the area of a standard square when $L=W$
 $= 2\lambda \times 2\lambda = 4\lambda^2$

$$C = \epsilon C_g [60\lambda^2/4\lambda^2] = 15 \times \epsilon C_g$$

In general, and is said to be common value of any layer with that dimensions

For a metal, relative capacitance is $0.075 \epsilon C_g$ and hence

$$= 15 \times 0.075 \epsilon C_g = 1.125 \epsilon C_g$$


For a polysilicon, relative capacitance is $0.1 \epsilon C_g$ and hence

$$= 15 \times 0.1 \epsilon C_g = 1.5 \epsilon C_g$$

For a diffusion, relative capacitance is $0.25 \epsilon C_g$ and hence

$$= 15 \times 0.25 \epsilon C_g = 3.75 \epsilon C_g$$

Some area Capacitance calculations

 

Some area Capacitance calculations: Example

$$C = \square C_g (A/A_\square)$$

Here, the structure is specified with three different layers. Such as

- i) Metal with $L=100\text{\AA}$ and $W=3\text{\AA}$ and hence $A_{\text{metal}}=3\text{\AA}\times 100\text{\AA}=300\text{\AA}^2$
- ii) Poly with $L=4\text{\AA}$ and $W=4\text{\AA}$, $L=2\text{\AA}$ and $W=2\text{\AA}$, and $L=1\text{\AA}$ and $W=2\text{\AA}$ hence $A_{\text{poly}}=(4\text{\AA}\times 4\text{\AA})+(2\text{\AA}\times 2\text{\AA})+(2\text{\AA}\times 1\text{\AA})=22\text{\AA}^2$
- iii) Diffusion with $L=2\text{\AA}$ and $W=2\text{\AA}$, $L=2\text{\AA}$ and $W=2\text{\AA}$ and hence $A_{\text{diffusion}}=(2\text{\AA}\times 2\text{\AA})+(2\text{\AA}\times 2\text{\AA})=8\text{\AA}^2$

$A_\square$ is the area of a standard square when $L=W=2\text{\AA}\times 2\text{\AA}=4\text{\AA}^2$

As an example, in 2um Technology, the capacitance value is calculated as

For a metal, relative capacitance is $0.075\square C_g$ and hence

$$C_{\text{metal}} = \square C_g [300\text{\AA}^2/4\text{\AA}^2] = 75\square C_g = 75\times 0.075\square C_g = 5.625\square C_g$$

For a polysilicon, relative capacitance is $0.1\square C_g$ and hence

$$C_{\text{poly}} = \square C_g [22\text{\AA}^2/4\text{\AA}^2] = 5.5\square C_g = 5.5\times 0.1\square C_g = 0.55\square C_g$$

For a diffusion, relative capacitance is $0.25\square C_g$ and hence

$$C_{\text{diffusion}} = \square C_g [8\text{\AA}^2/4\text{\AA}^2] = 2\square C_g = 2\times 0.25\square C_g = 0.5\square C_g$$

For a gate, relative capacitance is $1\square C_g$ and hence

$$C_{\text{gate}} = 1\square C_g$$

The total capacitance of the given structure is then

$$C = C_{\text{metal}} + C_{\text{poly}} + C_{\text{diffusion}} + C_{\text{gate}} = 7.675\square C_g$$

3. The Delay Unit

- **The delay unit:** The delay unit τ or a standard delay is defined as “the product of unit area capacitance and a unit n-channel sheet resistance R_s ”.
- The τ is used as fundamental time unit and all timings in a system can be assessed in relation τ
- by $\tau = 1.R_s \times 1.\square C_g$
- R_s value and $\square C_g$ value depends on the type of technology that is being used by the designer

Ex 1: for a 5 um Technology MOS structure;

Area of a standard square is $5\text{um} \times 5\text{um} = 25 \text{um}^2$

For 5um Technology:

$1.R_s = 10^4 \text{ ohms}$ and $1.\square C_g = 0.01\text{pF}$

Capacitance = $4 \times 10^{-4} \text{ pF/um}^2$

Thus the standard unit of capacitance


$$\square C_g = C_g \cdot A_{\square} = 4 \times 10^{-4} \text{ pF/um}^2 \times 25 \text{um}^2 = 0.01\text{pF}$$

Inverter pair delays

- In a pair of cascaded inverters, the delay over pair will be constant irrespective of logic level transmission at the input to output and is given by

$$T_d = \tau \left[1 + \frac{Z_{pu}}{Z_{pd}} \right]$$

 
$$T_d = \tau \left[1 + \frac{4}{1} \right]$$



- For a given inverter with (4:1 as $Z_{pu} : Z_{pd}$), the inverter pair delay is given by
 $= 5\tau$
- Here we need to have $R_{sp}=4 R_{sn}$ and $L_{pu}=4L_{pd}$
- In nMOS inverter, the delay is less than the delay in CMOS inverter ,because in CMOS the input is connected to both pMOS and nMOS and hence

$$C=2 \ C_g$$

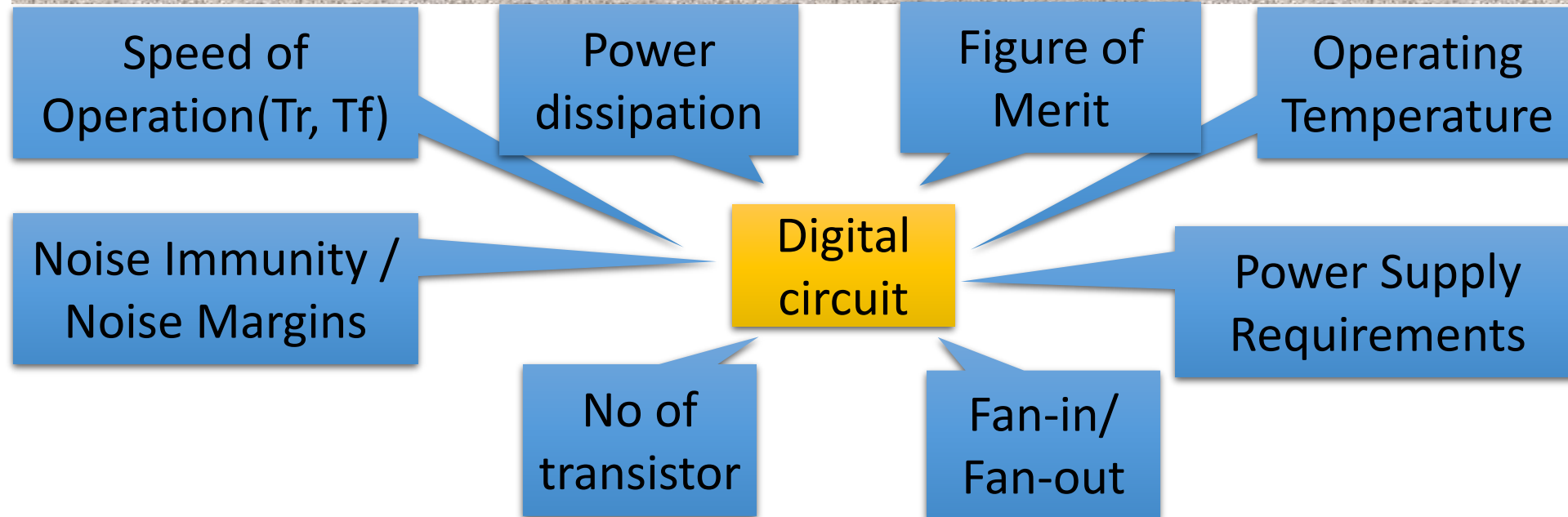The Performance parameters digital circuits



Formal estimation of CMOS inverter delay

The delay associated with the CMOS inverter can be more precisely estimated by splitting the output transition from input into rise time and fall time corresponding to the charging and its discharging of the capacitive load C_L .


The Switching speed of the CMOS gate is limited by time taken to charge and discharge the load capacitance C_L . Out of the list, Rise time, Fall time and propagation delay are the primary important.

- **Rise time (T_r)** is the time, during transition, when output switches from 10% to 90% of the maximum value.
- **Fall time (T_f)** is the time, during transition, when output switches from 90% to 10% of the maximum value.



Many designs could also prefer 30% to 70% for rise time and 70% -to-30% for fall time.

It could vary up to different designs.

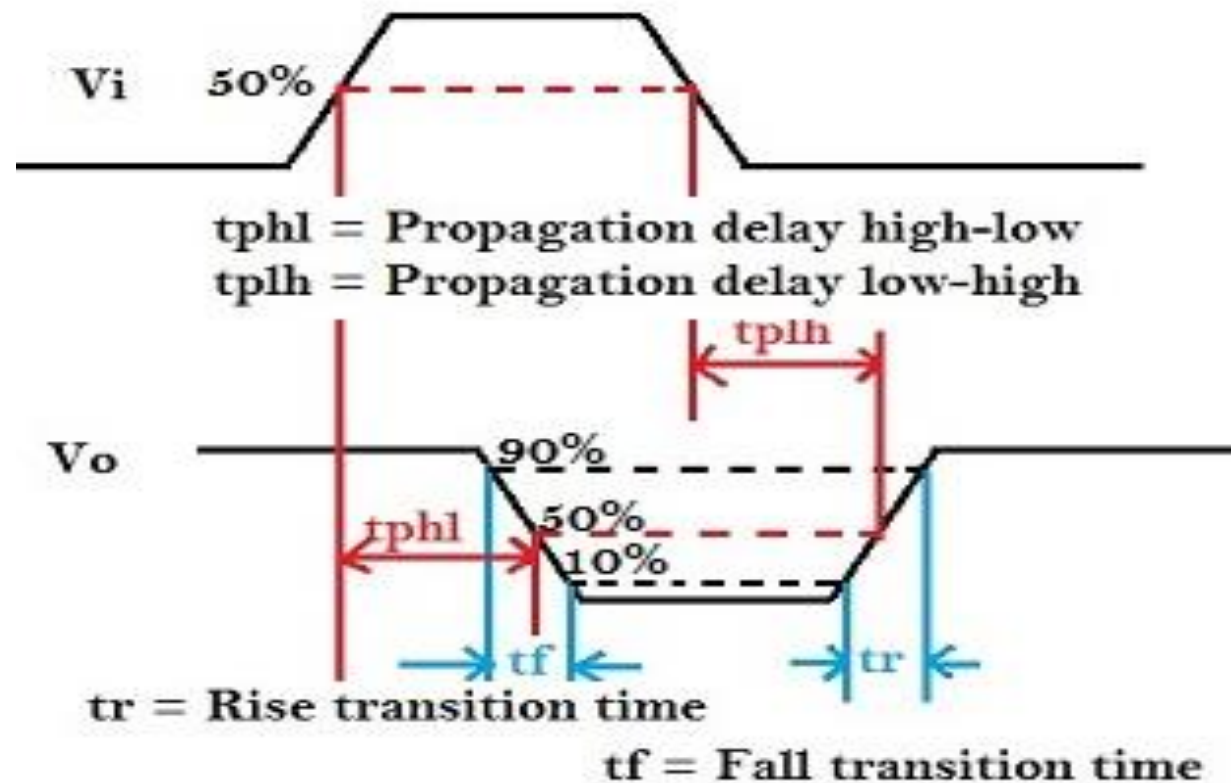
The propagation delay of a logic gate is the difference in time (calculated at 50% of input-to-output transition), when output switches, after application of input




Propagation delay & derivation

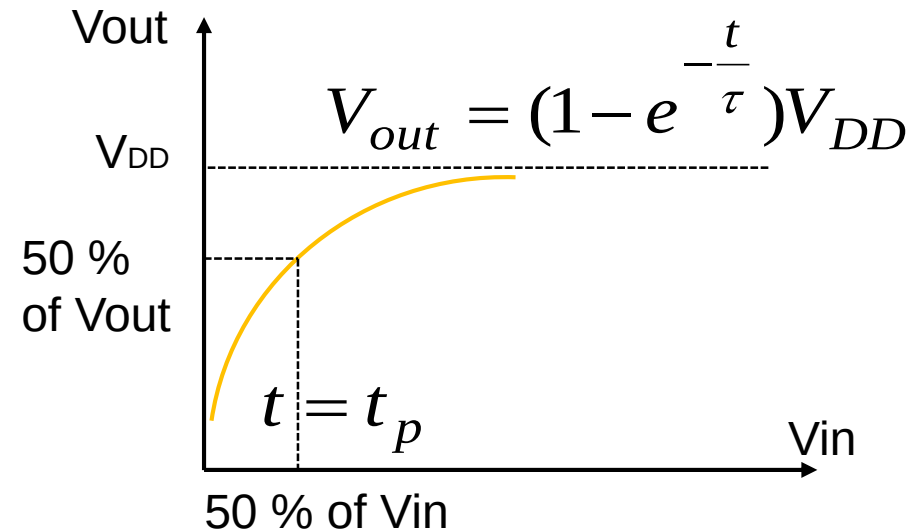 

- Our aim is to find 't' at $V_{DD} / 2$.
- $V_{out} = (1 - e^{-t/\tau}) V_{DD}$, where $\tau = RC = \text{time constant}$.
- Substituting ' V_{out} ' equal to $V_{DD}/2$, and ' t ' equal to ' t_p ' in above eq'n, $V_{DD}/2 = (1 - e^{-t_p/\tau}) V_{DD}$
- Therefore, $t_p = \ln(2) \tau = 0.69\tau$ whence, $t_p = 0.69RC$
- Hence, a CMOS inverter can be modeled as an RC network,
- Where $R = \text{Average 'ON' resistance of transistor \&}$
 $C = \text{Output or load Capacitance}$

 

Rise time model, C_L charges to V_{DD}

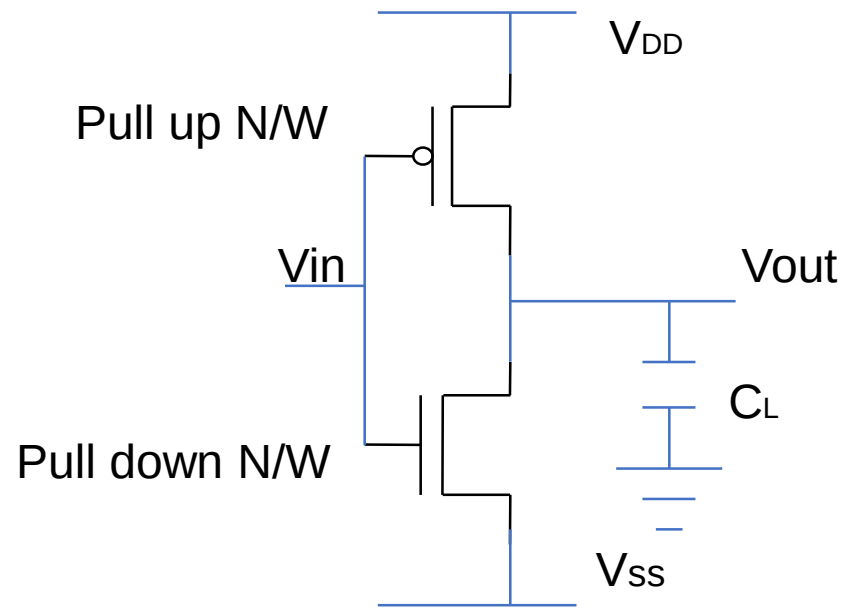

Fall time model, C_L discharges to V_{SS}

Rise time and fall time estimation

The current that is passing through pMOS transistor when it is in saturation is given by

$$I_{dsp} = \beta_p \left[\frac{(V_{gs} - |V_{tp}|)^2}{2} \right]$$

The output voltage across the load capacitance is given by

$$V_{C_L} = \frac{1}{C_L} \int I_{dsp} dt \quad \text{or} \quad V_{C_L} = \frac{1}{C_L} I_{dsp} \int dt \quad \Rightarrow \quad V_{C_L} = \frac{I_{dsp}}{C_L} t$$

Here
 $V_{gs} = V_{DD}$ and
 $V_{tp} = -0.2V_{DD}$

$$\Rightarrow t = \frac{V_{C_L} \cdot C_L}{I_{dsp}} = \frac{V_{out} \cdot C_L}{I_{dsp}} \quad \Rightarrow \quad t = \frac{2 \cdot V_{out} \cdot C_L}{\beta_p (V_{gs} - |V_{tp}|)^2}$$

T=tr when Vout=Vdd, and hence $\Rightarrow t_r = \frac{2 \cdot V_{DD} \cdot C_L}{\beta_p (V_{gs} - |V_{tp}|)^2} \Rightarrow t_r = \frac{2 \cdot V_{DD} \cdot C_L}{\beta_p (V_{DD} - |0.2V_{DD}|)^2}$

- And hence

$$\Rightarrow t_r = \frac{2.V_{DD}.C_L}{\beta_p (1-|0.2|)^2 .V_{DD}^2} \Rightarrow t_r = \frac{2.C_L}{\beta_p (0.8)^2 V_{DD}}$$

$$\Rightarrow t_r = \frac{2.C_L}{\beta_p 0.64.V_{DD}}$$

$$\therefore t_r \cong \frac{3.C_L}{\beta_p .V_{DD}}$$

$$\therefore t_f \cong \frac{3.C_L}{\beta_n .V_{DD}}$$

As charging and discharging currents are equal

- The fall time is also given by
- The relation between tr and tf is given by $\frac{t_r}{t_f} = \frac{\beta_n}{\beta_p}$ and are not same because of β_n and β_p


- Here $\beta_n = 2.5 \beta_p$ (Since $\mu_n = 2.5 \mu_p$) and hence $t_r = 2.5 t_f$
- The analytical models (shown above) are used for rise time and fall time estimation and will give the optimistic results. However ,
 - The tr and tf are proportional to CL
 - The tr and tf are proportional to 1/VDD and
 - for equal NMOS and PMOS $t_r = 2.5 t_f$

4. Wiring Capacitances

- In a circuit the capacitances are due to the following:

input capacitance, **output capacitance**, **wire capacitance** and **gate capacitance**(as shown)

 
In a MOSFET, the associated Capacitive components are shown in below figure, which are due to layer to substrate (poly, metal and diffusion) and gate to channel capacitances respectively.



- Out of which wiring capacitance is very significant source of capacitance and is arising due to the following ;
 - Fringing field(C_{ff}) or side wall capacitance.
 - Interlayer capacitance (inside MOS).
 - Peripheral capacitance(outside MOS)
- The fringing field or sidewall capacitance can be modelled as



$$C_{gf} = k_1 \frac{2\beta W}{\pi} \cosh^{-1} \left(\frac{T_{ox} + T_g}{T_{ox}} \right)$$

 - Where
 - C_{gf} is gate-to-electrode
 - C_{of} is gate-to-dielectric
 - β is scaling factor
- Channel or wire capacitance can be calculated in general



Fan in & Fan out characteristics

- Fan in is a term used to describe the maximum number of inputs which can be given to a logic gate (logic circuit). For example: A 3-input NAND gate has fan in equal to 3.
- Fan out is a term used to describe the maximum number of gates, an output of another gate (say gate A) can feed i.e how many other gates a single gate can drive.
- Therefore fan out here is mentioned for gate A, that gate which is giving its output as input to other. In the fig below, fan out of NOT gate is mentioned. Not gate can feed less than 4 gates but maximum number of gates it can feed is 4.

  


Scaling of MOS Circuits

➤ Scaling models & Scaling factors for device parameters

Subsystem Design

 - Architectural issues,
- Switch logic, Gate logic,
- Examples of structured design,
- Clocked sequential circuits
- System considerations,
- General considerations of subsystem design processes,
- An illustration of design processes



What is Scaling?

- Proportional adjustment of the dimensions of an electronic device while maintaining the electrical properties of the device, results in a device either *larger* or *smaller* than the un-scaled device.

Why Scaling?...

- Scale the devices and wires down, Make the chips ‘fatter’ – functionality, intelligence,
- memory – and – faster, Make more chips per wafer – increased yield, Make the end user happy

Scaling is characterized in terms of several indicators:

- Minimized feature size or increased number of gates on one chip,
- Reduced power dissipation ,
- Maximum operational frequency ,
- Reduced Production cost
- Fast SOC or NOC design

Scaling of Models and scaling factors:

$$I_{ds} = \frac{\epsilon_{ins}\epsilon_0}{D} WL \cdot \mu_n \cdot \frac{1}{L^2} \left([V_{gs} - V_t] - \frac{V_{ds}}{2} \right) \cdot V_{ds}$$


$$I_{ds} = C_g \cdot \mu_n \cdot \frac{1}{L^2} \left([V_{gs} - V_t] - \frac{V_{ds}}{2} \right) \cdot V_{ds}$$

- The most commonly used models are
 - Constant electric field scaling model
 - Constant voltage scaling model or
 - Hybrid scaling (voltage & dimension) model
- In order to accommodate the three models, two scaling factors $-1/\alpha$ and $-1/\beta$ are used;
- $1/\beta$ is a scaling factor used for supply voltages and Oxide thickness(V and D)
- $1/\alpha$ is a scaling factor used for all other linear dimensions
- For the constant field model and the constant voltage model, $\beta = \alpha = 1$
- The current/voltage is given by

$$\text{or } I_{ds} = C_0 \mu_n \cdot \frac{W}{L} \left([V_{gs} - V_t] - \frac{V_{ds}}{2} \right) \cdot V_{ds}$$

Scaling of Models and scaling factors:

- The most commonly used models are
 - Constant electric field scaling model
 - Constant voltage scaling model or
 - Hybrid scaling (voltage & dimension) model
- **Constant Voltage (CV)**
 - voltage remains constant as feature size is reduced causes electric field in channel to increase
 - decreases performance
 - but, device will fail if electric field gets too large
- **Constant Electric Field (CE)**
 - scale down voltage with feature size keeps electric field constant
 - maintain good performance
 - but, limit to how low voltage can go

 

Supply voltages and oxide thickness are scaled by $1/\beta$

Where as, all other parameters MOSFET are scaled by $1/\alpha$

Scaling factors for device parameters:

It is important that you understand how the following parameters are effected by scaling

- Gate Area
- Gate Capacitance per unit area
- Gate Capacitance
- Charge in Channel
- Channel Resistance
- Transistor Delay
- Maximum Operating Frequency
- Transistor Current
- Switching Energy
- Power Dissipation Per Gate (Static and Dynamic)
- Power Dissipation Per Unit Area
- Power - Speed Product

Scaling factors for device parameters:

- From the MOSFET characteristic equations, we may get the factors as:

➤ **Gate area (A_g):** the gate area of a MOS device is given by $A_g = WL$

- Both are scaled by $1/\alpha$

- And hence the gate area A_g is scaled by $1/\alpha^2$

➤ **Gate capacitance per unit area (C_o or C_{ox}):**


- The gate capacitance of a MOS device is given by $C_o = C_{ox} = \epsilon_{ox}/D$

- D is scaled by $1/\beta$ and hence capacitance is scaled by $1/(1/\beta) = \beta$

➤ **Gate capacitance (C_g):**

- The gate capacitance or total capacitance C_g is given by $C_g = C_o WL$

-

 -  C_o scaled by β
 W scaled by $1/\alpha$
 L scaled by $1/\alpha$

Hence C_g is scaled by β/α^2

➤ Parasitic capacitance (C_x):

- The parasitic capacitance of a MOS device is given by


$$C_x = (\epsilon_x A_x) / t$$

- A_x is scaled by $1/\alpha$ and t is scaled by $1/\alpha$
- Hence C_x is scaled by $1/\alpha$

➤ Carrier density in channel (Q_{on}):

- The carrier density in channel or charge in the channel is given by

$$Q_{on} = C_o V_{gs}$$

 -  C_o scaled by β
 V_{gs} scaled by $1/\beta$
Hence the Q_{on} is scaled by 1

➤ The channel resistance (R_{on}):

- The channel resistance R_{on} is given by

$$R_{on} = \frac{L}{W} \frac{1}{Q_{on}\mu}$$

- L, W scaled by $1/\alpha$
 - Qon scaled by 1
 And hence R_{on} is scaled by 1

➤ Gate delay (T_d):

- The gate delay is given by $T_d = R_{on}C_g$

- C_g is scaled by β/α^2
 - R_{on} scaled by 1
 And hence T_d is scaled by β/α^2

➤ Maximum operating frequency ($f_o = 1/T_d$):

- The operating frequency is scaled by α^2/β

➤ Saturation current (I_{dss}):

$$\Rightarrow I_{ds} = C_0 \mu_n \cdot \frac{W}{L} \left([V_{gs} - V_t] - \frac{V_{ds}}{2} \right) \cdot V_{ds}$$

$$\Rightarrow I_{ds} = \frac{C_0 \mu_n}{2} \frac{W}{L} (V_{gs} - V_t)^2$$

$$\Rightarrow I_{ds} = \frac{C_0 \mu_n}{2} \frac{W}{L} (V_{ds})^2$$

- Hence the I_{ds} is scaled by $\beta \cdot \frac{1}{\alpha} \cdot \frac{1}{1/\alpha} \cdot \frac{1}{\beta^2} = \frac{1}{\beta}$

For Co
For W
For L
For V_{ds}

- Current density (J):** current density J is given by I_{ds}/A

- {

I_{ds} scaled by $1/\beta$

And hence J is scaled by

A is scaled by $1/\alpha^2$

$$\frac{\frac{1}{\beta}}{\frac{1}{\alpha^2}} = \frac{\alpha^2}{\beta}$$

- Advantages and **disadvantages** with MOSFET scaling:

- ✓*** short channel effects(DIBL & hot electrons)
- ✓*** complex process technology
- ✓*** dominant parasitic effects

Observations on Device scaling

- Gate capacitance per micron is nearly independent of process
- But ON resistance * micron improves with process
- Gates get faster with scaling (good)
- Dynamic power goes down with scaling (good)
- Current density goes up with scaling (bad)
- Velocity saturation makes lateral scaling unsustainable

Limitations of scaling:

- Limits of miniaturization
- Limits of interconnect and contact resistance
- Limits due to sub-threshold currents:

With technology scaling, threshold voltage has to be scaled along with supply voltage, in order to maintain performance

Reduction in V_{th} increases the sub-threshold leakage current significantly

Sub-threshold leakage is the current that flows between the source and drain of a MOSFET when the transistor is in the weak-inversion region.

Sub-threshold leakage power will increase at a very rapid rate due to its strong dependence on the V_{th}

- Substrate doping
- Limits on logic levels and supply Voltage due to noise
- Limits due to current density


Subsystem Design

- Architectural issues,
- Switch logic & Gate logic,
- Examples of structured design,
- Clocked sequential circuits,
- System considerations,
- General considerations of subsystem design processes,
- An illustration of design processes.


Architectural issues: concepts applied in larger system design requirements

- Define the requirements (properly & carefully).
- Partition the overall architecture into appropriate subsystem.
- Consider communication paths carefully in order to develop sensible interrelationships between subsystem.
- Draw a floor plan of how the system is to map onto the silicon (and alternate between 2,3 and 4 as necessary).
- Aim for regular structures so that design is largely a matter of replication.
- Draw suitable (stick or symbolic) diagrams of the leaf_cells of the subsystems.
- Convert each cell to layout.

 
Switch logic & Gate logic: PT logic Examples



nMOS

 

pMOS

 

$$V_{out} = V_{in} - V_t$$

If $V_{in} = 0V$ then $V_{out} = 0 - V_{tn}$
 $= -V_{tn}$
 $\leq 0V$

Strong 0

If $V_{in} = 0V$ then $V_{out} = 0 - (-V_{tp})$
 $= +V_{tp}$
 $> 0V$

Weak 0

If $V_{in} = 5V$ then $V_{out} = 5V - V_{tn}$
 $< 5V$


Weak 1

If $V_{in} = 5V$ then $V_{out} = 5V - (-V_{tp})$
 $= 5V + V_{tp}$
 $\geq 5V$

Strong 1



- nMOS passes a good low (0) but not a good high (1)
- pMOS passes a good high (1) but not a good low (0)

 Switch logic & Gate logic: PT logic Examples






Vout=Vin; when A=B=C=D=1

Vout logic levels will be degraded by Vt

 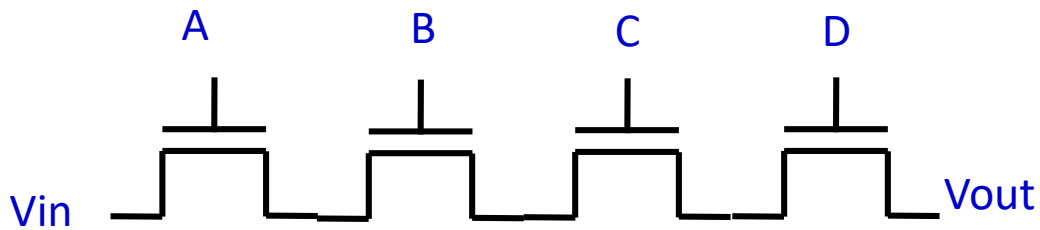


AND gate with PT logic

 
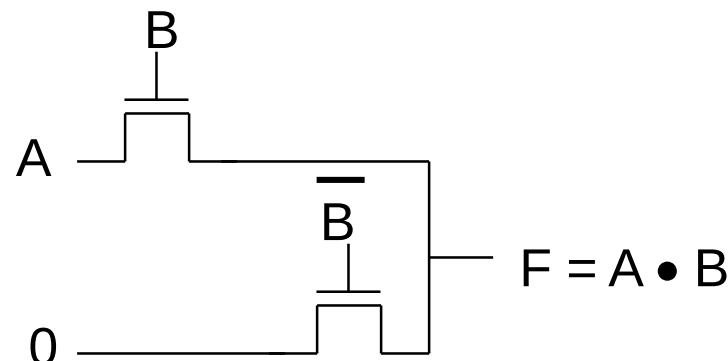
 


F = A . B

 
Switch logic & Gate logic: TG logic Examples



 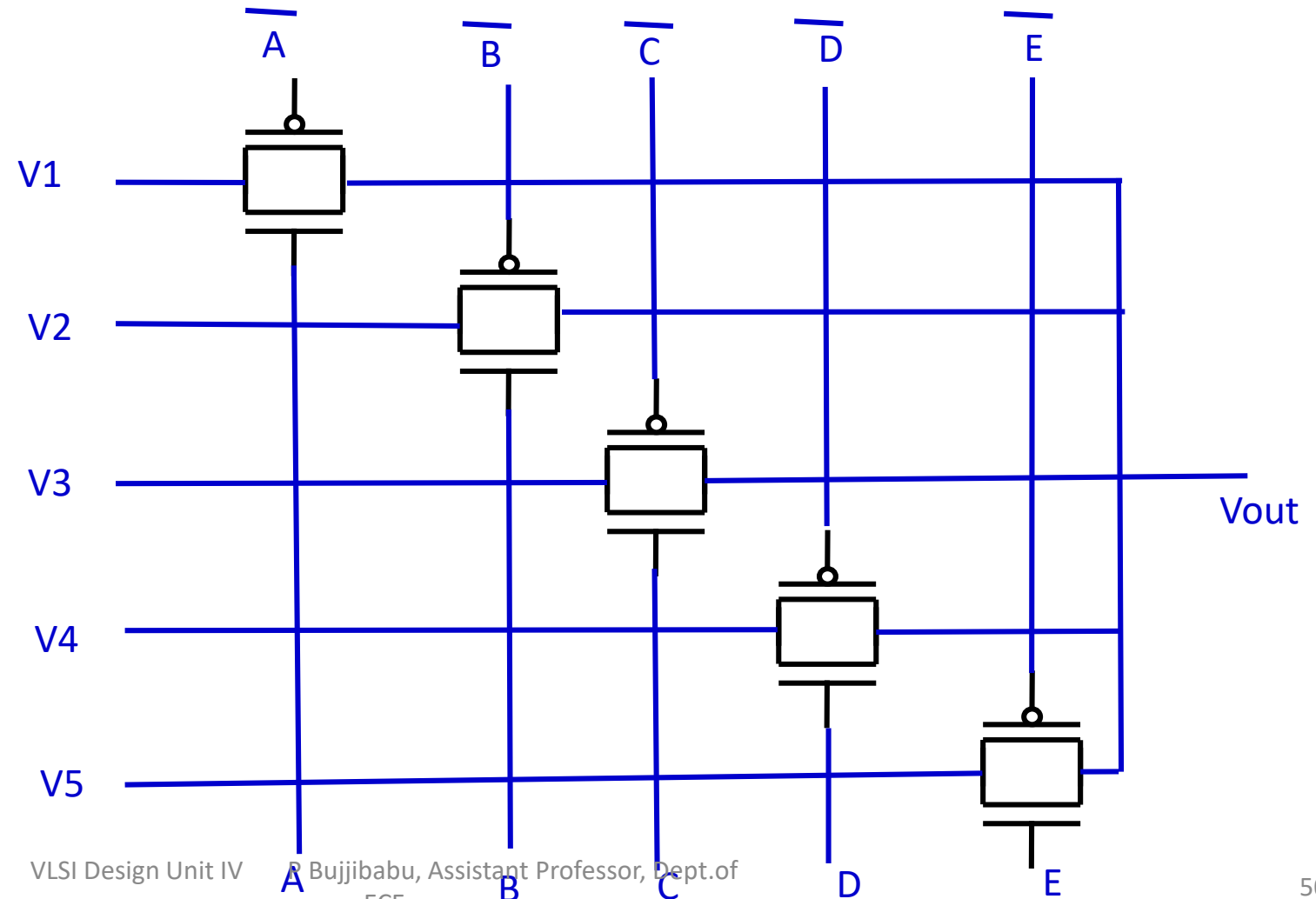 
NMOS passes a strong "0" PMOS passes a strong "1"
TG-enable rail-to-rail swing-passes a strong "0" and a strong "1"
These gates are particularly efficient in implementing MUXs



Switch logic & Gate logic

 

Switch logic & Gate logic

 


Schematics(different types)can be...

1. Logic with Resistor as PU
2. CMOS Logic
3. Logic with enhancement nMOS as PU
4. Logic with depletion nMOS as PU
5. Pseudo nMOS logic
6. Logic with enhancement pMOS as PD
7. Logic with depletion pMOS as PD
8. Dynamic CMOS Logic
9. Differential Cascade Voltage Switch Logic
10. CMOS Domino Logic
11. GDIL logic
12. Domino logic with pre charge
13. Clocked CMOS Logic (C^2 MOS).
14. NP Domino Logic (Zipper CMOS).
15. Source Follower Pull-up Logic (SFPL).

No of Transistors
changes and area
reduces & even power


16. circuits with MTCMOS/VTMOS logics

Switch logic & Gate logic

 

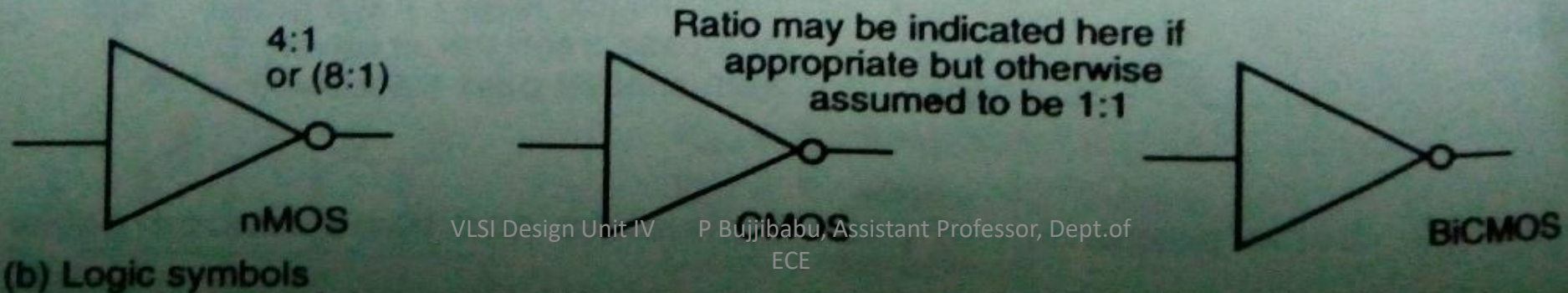
(a) Circuit symbols

(Note: n- and p-transistors assumed to be min. size unless stated otherwise.)




(b) Logic symbols

Switch logic & Gate logic

 


Switch logic & Gate logic

 


 (a) Circuit diagrams


Note: n- and p- transistors assumed to be minimum size unless stated otherwise.



Switch logic & Gate logic


 


Switch logic & Gate logic

 


Symbolic form (BiCMOS)


Switch logic & Gate logic

  


Switch logic & Gate logic

 


Switch logic & Gate logic

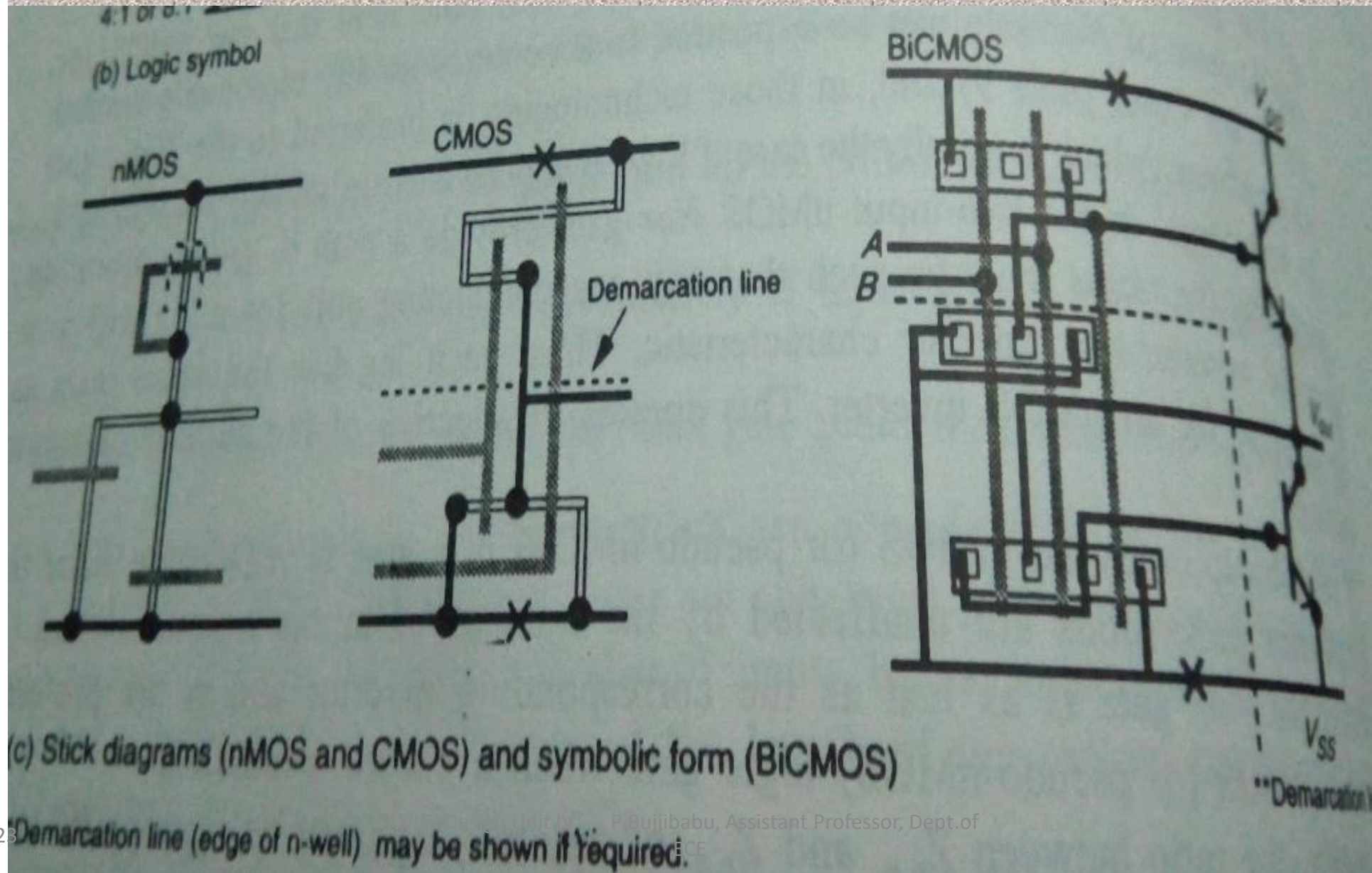


Switch logic & Gate logic

 


Switch logic & Gate logic

 

Switch logic & Gate logic

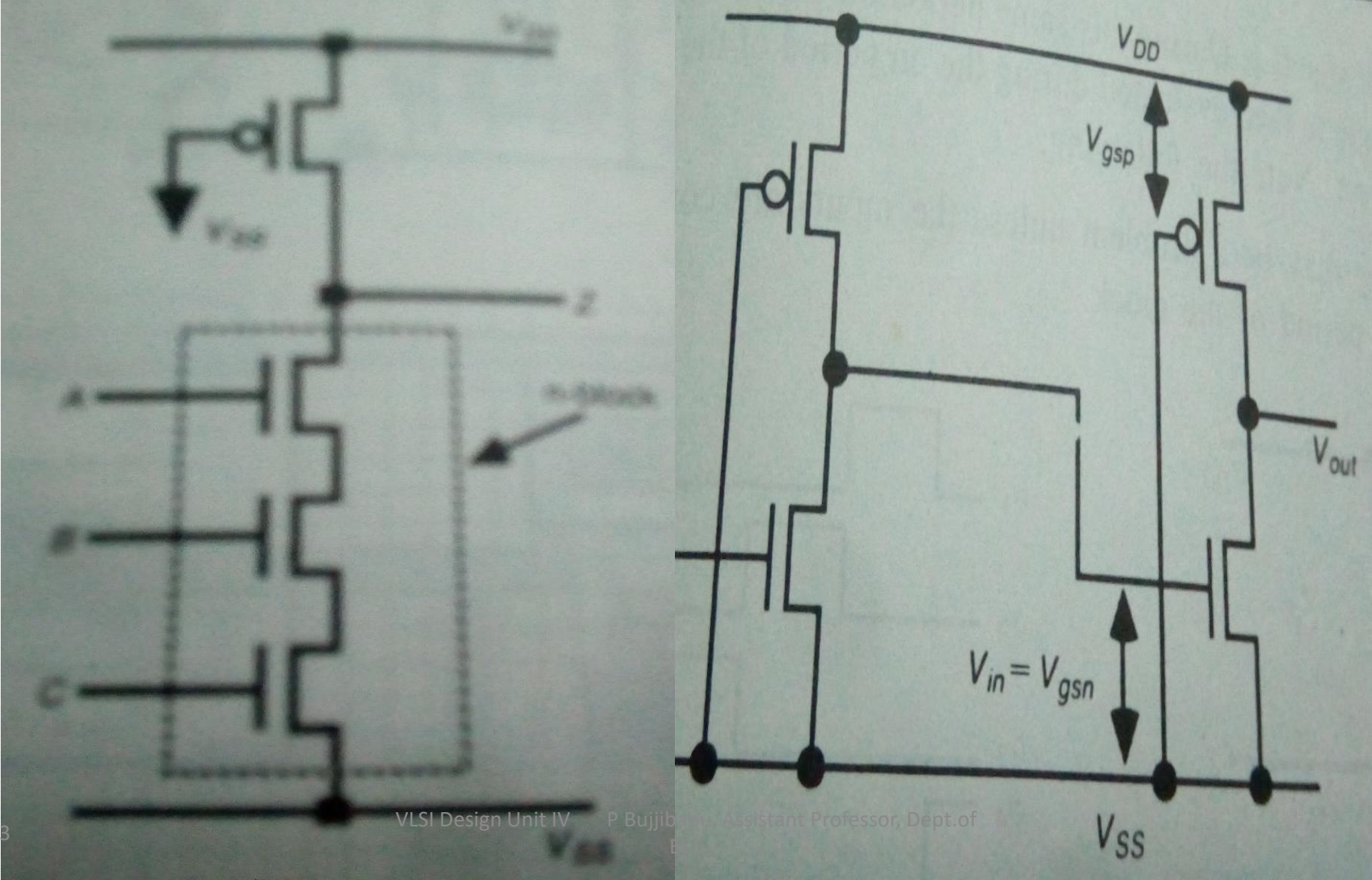


Switch logic & Gate logic

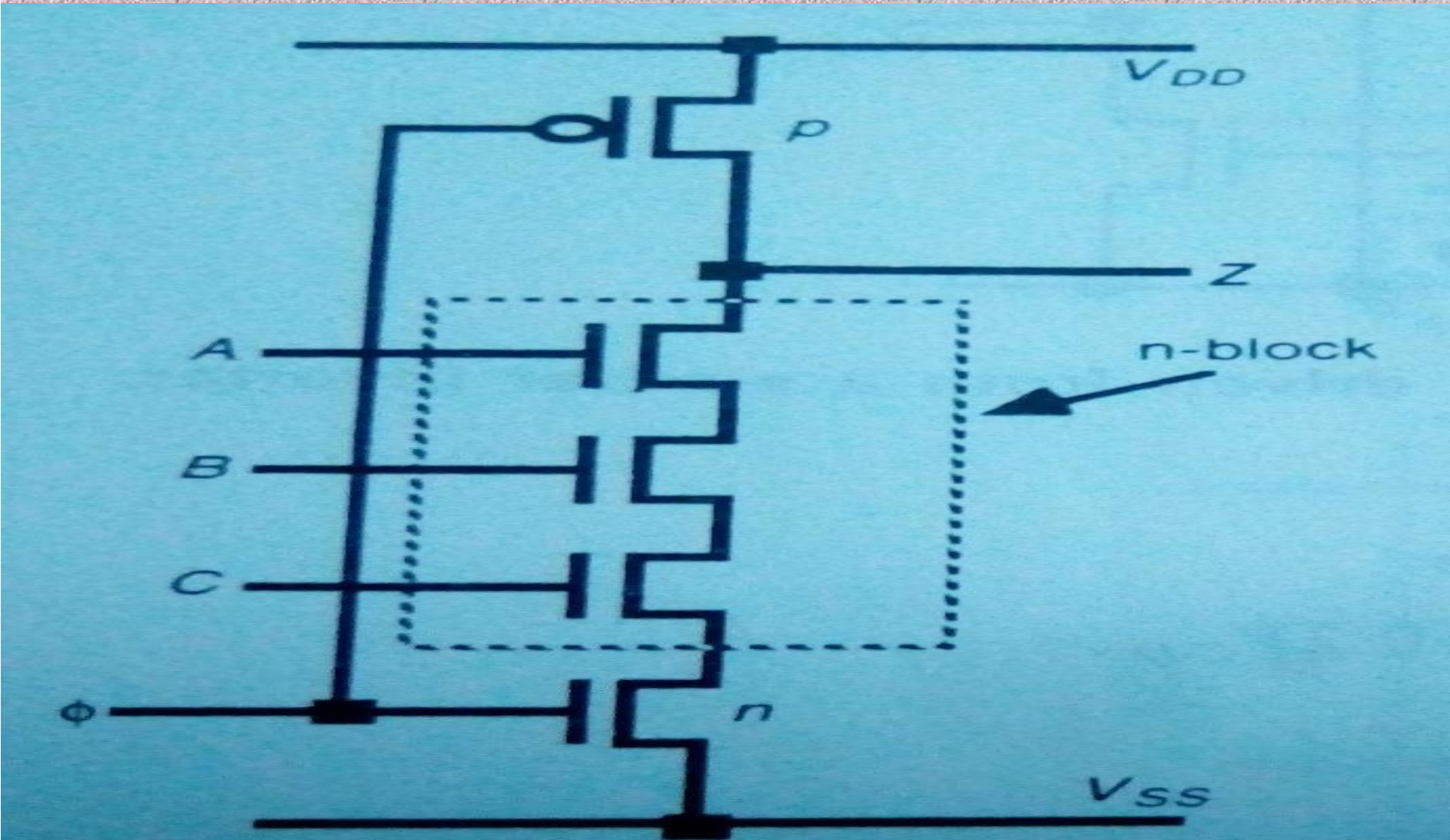

(a) Schematic


Gate logic: Clocked CMOS logic

 


(a) 2 I/P Nor gate

(b) Inverter


Gate logic: Domino logic

 

 
Examples of structured design, Adder RTL diagrams





Half adder using NOR logic

 


Half adder

 


Half adder using NAND logic

  

Full adder

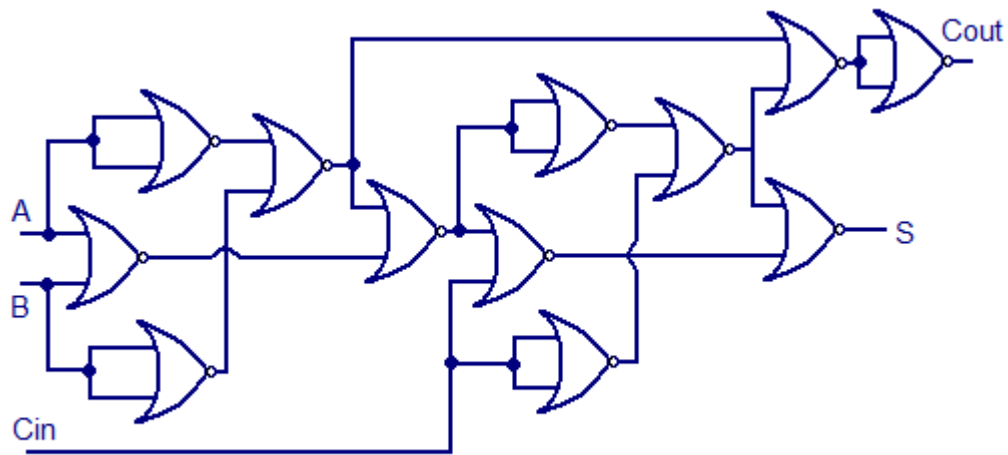



Full adder using NOR logic

 



Full adder using NAND logic

Structured Design


- Levels of abstraction-Y chart

  

Example of structured Design-4 bit adder

 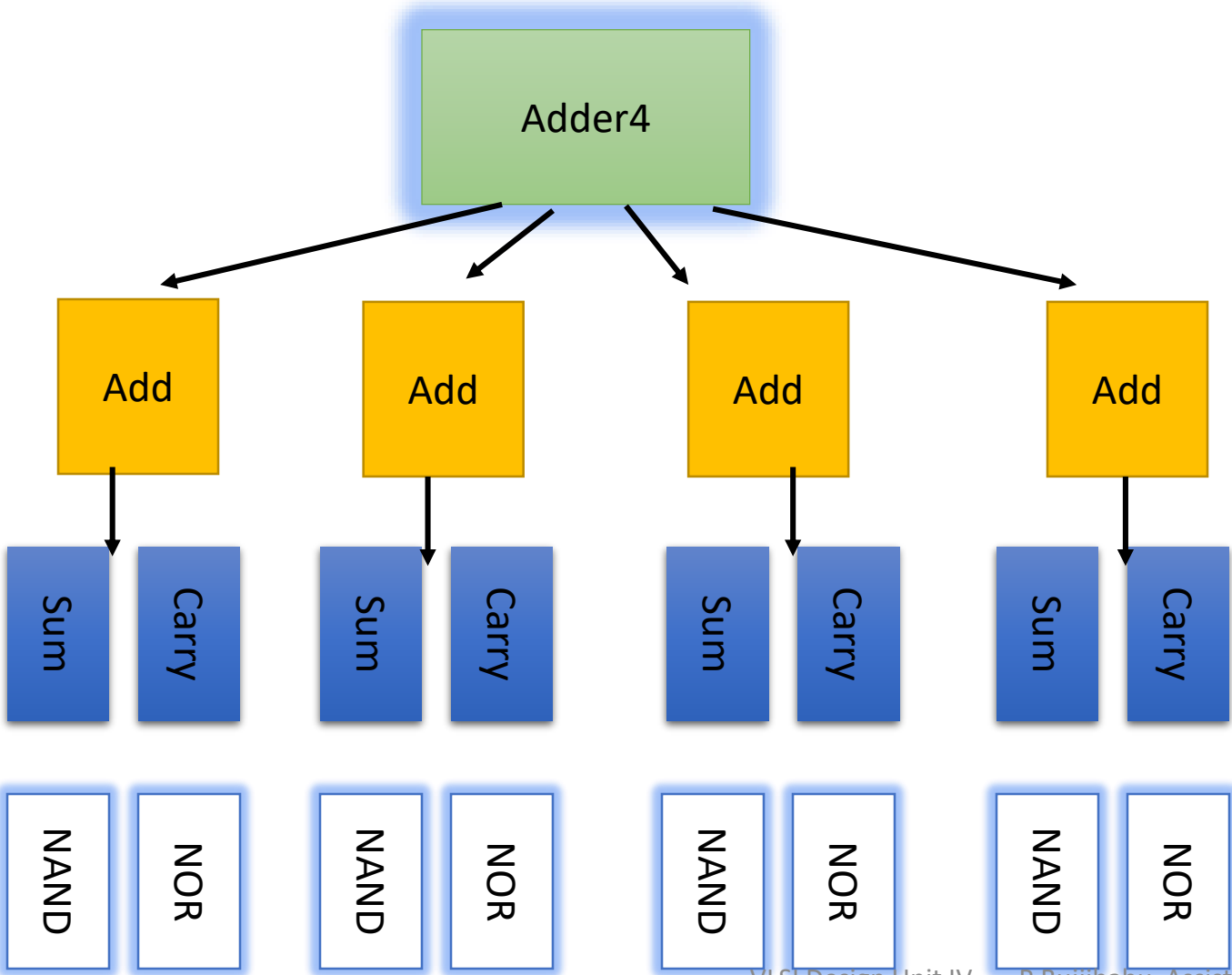

Hierarchical & Modular Layout

 

Example of structured Design

Design Strategies:

- Metrics for Design Success:
 - Performance Specs
 - logical function, speed, power, area
 - Time to Design
 - engineering cost and schedule
 - Ease of Test Generation and Testability
 - engineering cost, manufacturing cost, schedule
- Design is a continuous tradeoff to achieve performance specs with adequate results in the other metrics
- **Hierarchy:** Subdivide the design in several levels of sub- modules
- **Modularity:** Define sub-modules unambiguously and well defined interfaces
- **Regularity:** Subdivide to max number of similar sub- modules at each level
- **Locality:** Max local connections, keeping critical paths within module boundaries

Examples of structured Design


ALU

Parity Generator(or xor gate)

Bus arbitration logic- or control logic

Ect...

An illustration of Design process: ALU

 


```
module ALUwithIPCORE(  
    input [7:0] A,B, // ALU 8-bit Inputs  
    input [3:0] ALU_Sel, // ALU Selection  
    output [7:0] ALU_Out, // ALU 8-bit Output  
    output CarryOut // Carry Out Flag  
);
```

```
reg [7:0] ALU_Result;  
wire [8:0] tmp;  
assign ALU_Out = ALU_Result; // ALU out  
assign tmp = {1'b0,A} + {1'b0,B};  
assign CarryOut = tmp[8]; // Carryout flag
```



An illustration of Design process: ALU

```
always @(*)
begin
  case(ALU_Sel)
    4'b0000: // Addition
      ALU_Result = A + B ;
    4'b0001: // Subtraction
      ALU_Result = A - B ;
    4'b0010: // Multiplication
      ALU_Result = A * B;
    4'b0011: // Division
      ALU_Result = A/B;
    4'b0100: // Logical shift left
      ALU_Result = A<<1;
    4'b0101: // Logical shift right
      ALU_Result = A>>1;
    4'b0110: // Rotate left
      ALU_Result = {A[6:0],A[7]};
    4'b0111: // Rotate right
      ALU_Result = {A[0],A[7:1]};
```



```
4'b1000: // Logical and
  ALU_Result = A & B;
4'b1001: // Logical or
  ALU_Result = A | B;
4'b1010: // Logical xor
  ALU_Result = A ^ B;
4'b1011: // Logical nor
```

 

An illustration of Design process: ALU

  

An illustration of Design process: ALU

  

Working with FPGA-With the core

In a case, where total number of input/output pins are very high(not possible to observe the output without additional modules) then the core usage is required.

Now for a complex module, it is always recommendable to workout the issue with the help of creating the IP cores(ie...VIO, ILA);


- Complete the description in HDL(VHDL or Verilog) for a your logic.
- Verify its functional response through simulation.
- Create the cores with the total no. of modules sufficient to interface required set of inputs and outputs.
- Add the constraints (XDC) file (*get it from device vendor's website)
 - In general, it is from <https://github.com/Digilent/digilent-xdc/>, for Digilent FPGA family
 - Bords- like., **ARTIX 7-XC7A35Tftg256-1**
- Carry out the Synthesis, Implementation and generate the bit file.
- Connect the corresponding h/w Board.
- Dump the bit file with the help of JTAG cable
- Verify the functional response with the VIO and ILA control signals through the Board

An illustration of Design process: ALU

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power: 0.071 W
Design Power Budget: Not Specified
Power Budget Margin: N/A
Junction Temperature: 25.3°C
 Thermal Margin: 59.7°C (12.2 W)
 Effective θ_{JA} : 4.9°C/W
 Power supplied to off-chip devices: 0 W
 Confidence level: Low

On-Chip Power

 

Setup

Worst Negative Slack (WNS): 26.931 ns
 Total Negative Slack (TNS): 0.000 ns
 Number of Failing Endpoints: 0
 Total Number of Endpoints: 1041

Hold

Worst Hold Slack (WHS): 0.021 ns
 Total Hold Slack (THS): 0.000 ns
 Number of Failing Endpoints: 0
 Total Number of Endpoints: 1033

Pulse Width

Worst Pulse Width Slack (WPWS): 15.250 ns
 Total Pulse Width Negative Slack (TPWS): 0.000 ns
 Number of Failing Endpoints: 0
 Total Number of Endpoints: 487

All user specified timing constraints are met.

Useful Web links:

<http://emicroelectronics.free.fr/onlineCourses/VLSI/toc.html>

http://ece-research.unm.edu/jimp/vlsi/slides/c1_its.pdf

<http://rti.etf.bg.ac.rs/rti/ri5rvl/tutorial/TUTORIAL/HTML/HOME.PG.HTM>

https://www.tutorialspoint.com/vlsi_design/vlsi_design_useful_resources.htm

<https://www.southampton.ac.uk/~bim/notes/cad/>

<http://www.uta.edu/ronc/4345sp02/lectures/>

http://www.ece.utep.edu/courses/web5392/Lab_7.html

<http://www.ece.utep.edu/courses/web5392/Notes.html>

<http://www.ittc.ku.edu/~jstiles/312/handouts/>

<https://www.mepits.com/tutorial/384/vlsi/steps-for-ic-manufacturing>

https://personalpages.hs-kempten.de/~vollratj/Microelectronics/2017_04_24_06_Micro_DesignRules.html