

1. The barrier voltage for germanium is 25degree
Ans: 0.3 v
2. Reverse saturation current.... For every 10 degree rise in temperature
Ans: Doubles
3. The center tapped full wave rectifiers efficiency is
Ans: 81.2%
4. TUF for a half wave rectifier and center tapped full wave rectifier is ---- and respectively.
Ans: 28.6%, 57.2%
5. The rectifier efficiency of a half-wave rectifier is if the input power to the rectifier is 150 W and output power is 50 W.
Ans: 33.33%
6. If input frequency is 100 Hz for a half-wave rectifier, the ripple frequency of it would be.
Ans: 100 Hz
7. The ripple factor for a half-wave rectifier without filter is.
Ans: 1.21
8. Which type of impurity is to added to a pure semi-conductor to get an n-type semiconductor?
Ans: Pentavalent impurity
9. The process of adding pentavalent and trivalent impurities to a pure semiconductor is called:
Ans: Doping
10. Which of the following materials has large number of free electrons in it?
Ans: Conductors
11. In an intrinsic semiconductor there are
Ans: Equal number of free electrons and holes
12. Which of the following has the highest mobility
Ans: Electron
13. The temperature co-efficient of an intrinsic semiconductor is—
Ans: Negative
14. Which of the following is tetravalent?
Ans: Germanium
15. The minority carrier concentration is largely a function of
Ans: Temperature
16. Which of the following element belongs to the same group of periodic tables as that of silicon and lead?
Ans: Carbon
17. Which of the following materials is a semiconductor?
Ans: Selenium
18. If an atom losses one or more electrons, it becomes.....
Ans: Electrically positive
19. Fermi energy level for n-type extrinsic semiconductors lies.....
Ans: Close to conduction band
20. In a semiconductor, the resistivity
Ans: Depends on temperature
21. To prepare a P-type semiconducting material the impurities to be added to silicon are?
Ans: Boron, Gallium
22. The impurity added to extrinsic semiconductors is of the order of
Ans: 1 in million
23. The number of valence electrons of P and Si are respectively?
Ans: 5 and 4
24. Which one of the following material has lowest resistivity?
Ans: Conductors
25. When an electron is removed from an atom, it becomes
Ans: ionized
26. The donor type of impurity is
Ans: Phosphorous
27. Which of the following is a trivalent?
Ans: All options are correct
28. What is the resultant charge in a body whenever the number of protons equal the number of electrons in it?
Ans: Zero charge
29. The basic shift register operation is :
Ans: All options are correct
30. The electrons in the outer most orbit of an atom are known as:
Ans: Valence electrons
31. The number of valence electron in boron is.....
Ans: 3
32. The plate current in a triode can be controlled by controlling.....
Ans: Grid voltage
33. The conductivity of silicon can be expected around:
Ans: $0.5 \times 10^{-3} \text{ S/m}$
34. A p-type semiconductor is
Ans: Uncharged

35. The drift velocity of electrons, in silicon.....

Ans: Increases linearly with electric field at low values of electric field and gradually saturates at higher values of electric field

36. Resistivity of a semiconductor depends on.....

Ans: The atomic nature of the semiconductor

37. A germanium atom contains.....

a) Four valence electrons

38. A hole is the vacancy created when.....

Ans: An electron breaks its covalent band

39. For bidden energy gap between valence band and conduction band is least in the case of.....

Ans: Impure silicon

40. Donor impurity atom in a semiconductor result in new.....

Ans: Discrete energy level just below conduction level

41. In a semiconductor, movement of charge carriers under influence of an electric field is called.....

Ans: Drift

42. In pure silicon, major part of the drift current is due to free electrons because.....

Ans: Mobility of electrons is greater than the mobility of holes

43. Semiconductor may be made n-type by adding donor impurity.....

Ans: During crystal pulling

44. Resistivity measurements are often used to determine:

Ans: Carrier concentration in extrinsic semiconductor

45. In Ge, when atoms are held together by the sharing of valence electrons:

Ans: Valence electrons form reversible covalent bonds

46. In a pure semiconductor, electric current is due to:

Ans: Both holes and electrons

47. Accept or impurity atoms in a semiconductor result in new :

Ans: Discrete energy level just above valence level

48. A n-type semiconductor is:

Ans: Electrically neutral

49. When a free electron is recaptured by a hole,

the process is called:

Ans: Recombination

50. At room temperature intrinsic carrier concentration is higher in germanium than in silicon because:

Ans: Energy gap in Ge is smaller than in Si

51. Epitaxial grow this best suited for growing:

Ans: Very thin single crystal layer on a substrate

52. Which particles act as a current carrier in a metallic conductor?

Ans: Only electrons

53. The donor atoms in an N-type semiconductor at normal temperature:

Ans: Carry a positive charge

54. Consider a single crystal of an intrinsic semiconductor. The number of free carriers at the fermi level at room temperature is:

Ans: Half the number of free electrons in the crystal

55. When an electric current flows through a conductor, its temperature rises. This is because of.....

Ans: Collisions between conduction electrons and atoms

56. An electron device means the device in which the conduction of electrons takes place through.....

Ans: Gas, vacuum, semiconductor

57. Which of the following impurity is to be added in pure germanium to obtain p type semiconductor

Ans: Gallium

58. In silicon energy must be supplied to push the electron from valance band to conduction band.

Ans: 1.1 eV

59. Germanium Behaves as an insulator at temperature of

Ans: 0 K

60. Which of the following statement sis FALSE about LED lamps?

Ans: An LED is doped with silicon and germanium like all semiconductor devices

61. For a germanium diode having a forward current of 10 mA and 30ns as charge carrier transit time, the diffusion capacitance is.

b) 1 nF

62. The diffusion capacitance for a silicon diode with 20 mA forward current, if the charge carrier transit time is 70ns, is.

Ans: 2 nf

63. What is the number of diodes used in a bridge rectifier, full wave rectifier and half wave rectifier respectively?

Ans: 4, 2, 1

64. The value of form factor and ripple factor of a half wave rectifier are and respectively.

Ans: 1.57, 1.21

65. Choose the INCORRECT statement with regard to a forward biased pn diode.

Ans: The potential barrier is constant irrespective of magnitude of the applied voltage.

66. The potential barrier existing across pn junction.

Ans: Prevents flow of minority carriers

67. The diffusion potential across a p-n junction:

Ans: Increase with increase in doping concentrations

68. As compared to a full-wave rectifier using two diodes, the four diode bridge rectifier has the dominant advantage of:

Ans: Lower peak inverse voltage requirement

69. Frequency multiplication by a resistor can be achieved, if:

Ans: It is a diode

70. Applications of precision diode are:

- i. Half wave rectifier
- ii. Peak detector
- iii. Window detector

Ans: i, & ii

71. A device having characteristics very close to that of an ideal voltage source is.....

Ans: Zener diode

72. For the rm ionic emission.....

Ans: A material with low work function is Preferable

73. A photo cell is illuminated by a small bright source placed 1 meter away. When the same source of light is placed two meters away, the electrons emitted by the photo cathode.....

Ans: Are one-quarter as numerous

74. The depletion region of PN junction is consist of:

- c) IM Mobile charge

75. Which of the following terms is NOT associated With diodes?

Ans: Gate

76. Which of the following devices is used in voltage limiters as a fixed reference voltage in the network?

Ans: Zener diode


77. Transistor when working in the saturation region acts as and in the cut off region acts as.

Ans: Closed switch; open switch

78. Which of the following is used with a photo meter for the conversion of light into electric current?

Ans: Photo diode

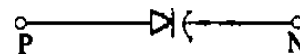79. Identify the device in the following symbol.



Ans: Varactor diode

80. Which of the following diode is also known as a volt cap or 'voltage-variable' 'capacitor diode'?

Ans: Varactor diode

81. The Ebers-Moll model is applicable to-

Ans: Bi polar junction transistors

82. In which of the following amplifier configurations, The power gain is the largest?

Ans: Common-Emitter

83. In an electronic circuit transistor is used for switching ON and OFF a relay, when the transistor switches OFF the relay, a higher voltage appears across the transistor. How can a transistor be protected from this voltage?

Ans: A diode parallel to the relay

84. For active region operation of NPN transistor

Ans: Emitter is negative with respect to base

85. The operating point is also called the:

Ans: Quiescent point

86. Transistor can be used to:

Ans: All options are correct

87. β gain of the transistor signifies:

Ans: Amplification capability of the transistor

88. In a vacuum tetrode secondary emission is because of emission of.....

Ans: Electrons from the plate due to bombardment of the fast moving electrons emitted from the cathodes

89. For normal operation of a transistor, the collector-base junction is—

Ans: Always reverse biased

90. The disadvantage of base resistor method of transistor biasing is that it

Ans: Is sensitive to changes in beta (β)

91. To operate properly a transistor's base-emitter junction must be forward biased with reverse bias applied to which junction?

Ans: Base-collector

92. With the positive probe on an NPN base, an ohm meter reading between the other transistor terminals should be?

Ans: Low resistance


93. A transistor can be made to operate as a switch by operating it in which of the following regions?

Ans: Saturation region, cut-off region

94. If the temperature increases, the value of V_{BE}

Ans: Is decreased

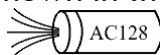95. In the figure below you see an electronic component. Which type of electronics component is shown in the figure?



Ans: Low power transistor

96. A transistor consists of.....

Ans: Two p-n junction

97. For normal operation of a transistor, the collector-base junction is—

Ans: Always reverse biased

98. α -Cut off frequency of bipolar junction transistor increase:

Ans: With the decrease in base width

99. What is the characteristics of an ideal voltage amplifier with respect to the input and output impedance?

Ans: High input and low output impedance


100. The collector circuit in a transistor amplifier circuit is.....

Ans: Reverse bias at all times

101. Which of the following circuit is mostly used as an amplifier

Ans: Common emitter circuit because it has high voltage and current gain

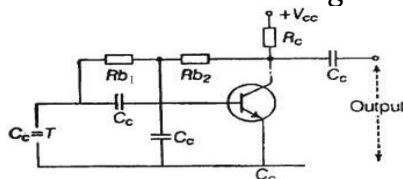102. What is the method of biasing used in the amplifier circuit shown in the figure?



Ans: Collector to base bias

103. For n-JFET, the channel is a/an channel and

gates are.

Ans: N type; P type

104. In an E-MOSFET, the surface is coated with.

Ans: Silicon dioxide

105. JFET is a/an device.

Ans: Unipolar


106. What kind of device is Field Effect Transistor?

Ans: Unipolar semiconductor

107. AFET is essentially a


Ans: Voltage driven device

108. Figure represents a

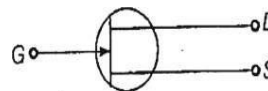

Ans: Junction field effect transistor

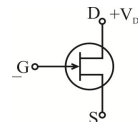109. Identify the device based on the given symbol



Ans: N-channel JFET

110. Choose the correct statement when $V_{GS} = 0$ and $V_{DS} = 0$ in a JFET.

Ans: The depletion regions around the p-n junctions are equal in thickness and symmetrical.

111. The threshold voltage of an n-channel MOSFET can be increased by.....

Ans: Reducing the gate oxide thickness

112. The transit time of the current carriers through the channel of an FET decides itscharacteristics:

Ans: Switching

113. An amplifier is used to obtain

Ans: An increased voltage, current or power of an input signal

114. The function of the emitter by pass capacitor in CE amplifier is

Ans: Provide a low resistance path for the AC signals

115. The current gain of common base amplifier is

Ans: Less than 1

116. What is the characteristics of common collector configuration amplifier with respect to the input and output impedance?

Ans: High input and low output impedance

117. The gain of a CE amplifier is highest at

Ans: Mid frequencies

118. The efficiency of the class B amplifier is Approximately?

Ans: 70% to 100%

119. The circuit that provides the best stabilization of operating point is:

Ans: Potential divider bias

120. The circuit that would be used for 455kHz, if amplifier is:

Ans: Double tuned transformer

121. NPN and PNP are types of:

Ans: Transistors

122. Input resistance of a common emitter transistor of the order of

Ans: 1 k Ω

123. In Bipolar Junction Transistors, the type of configuration which will give both voltage gain and current gain is:

Ans: CE

124. What is the position of the input and output signals of CE amplifier?

Ans: 180° out of phase

125. The CE amplifier is most commonly used because of.....

Ans: More power gain

126. What is the range of an FET's input impedance?

Ans: 1 M Ω to 100 M Ω

127. An amplifier has a gain of 10,000 expressed in decibels the gain is?

Ans: 40

128. In an RC coupled amplifier, low frequency response is improved with

Ans: Less gain

129. The type of circuit that does not need a coupling capacitor is

Ans: Transformer coupled

130. A semiconductor has a band gap of 2 eV. The wavelength of radiation emitted from the semiconductor when electrons and holes recombine is.....

Ans: 625 nm

131. In an RC-coupled common emitter amplifier: **Ans:** Both coupling and bypass capacitance affect the le response only

132. Class-A transformer coupled, transistor power amplifier is required to deliver a power output of 10 watts. The maximum power rating of the transistor should not be less than : **Ans:** 20W

133. Class AB operation is often used in power

(large signal) amplifiers in order to.....

Ans: Overcome a crossover distortion

134. _____ is the dominant form of distortion produced by the simple push-pull amplifier:

Ans: Crossover distortion

135. The advantage of negative feedback is

Ans: All of the above

136. Which of the following methods can result in a square waveform?

Ans: Multi vibrators

137. A tank circuit consists of

Ans: A pure inductance and a pure capacitance connected in parallel

138. An oscillator uses-

Ans: Positive feedback

139. The output time period of a transistorised mono-stable multi-vibrator using base resistor Rb and coupling Ct for the output transistor is given by

Ans: 0.69 RbCb

140. A current mirror can be used as an active load because.....

Ans: It has high AC resistance

141. In general, if a sine wave is fed into a Schmitt trigger, the output will be

Ans: A square wave

142. A special case of non-inverting amplifier in which all of the output voltage is fed back to the inverting input of the op-amp is called:

Ans: Voltage follower

143. Silicon has a preference in IC technology because?

Ans: Of the availability of nature oxide SiO₂

144. The number of slip rings of a single-phase and a three-phase converter are respectively.....

Ans: 2 and 6

145. A switched mode power supply operating at 20kHz to 100kHz range uses as the main switching element is :

Ans: MOSFET

146. Which of the following is NOT a disadvantage of the direct laying method?

Ans: Heat can be dissipated easily

147. Figure given below represents a



Ans: Unijunction transistor

148. Which one of the following is used as an active device in electronic circuits?

Ans: SCR

149. Which of the following diodes is a PNPN device with two terminals

Ans: Light emitting diode

150. TRIAC is equivalent to

Ans: Two SCRs connected in parallel

151. 4F2D is a/an number


Ans: Octal

152. In the below circuit, $X=?$




Ans: A.B

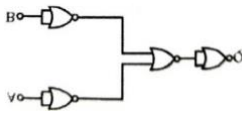153. The output of logic circuit given below represents




Ans: NAND

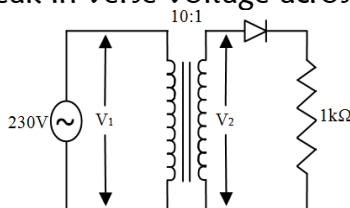154. An AC supply of 230 V is applied to half-wave rectifier through transformer of turns ratio 10 : 1 as shown in figure. Determine the peak inverse voltage across the diode.



Ans: 32.5V

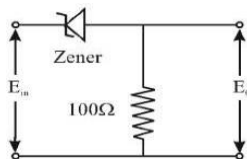155. Find the output voltage of the given network if $E_{in} = 6\text{ V}$ and the Zener breakdown voltage of the Zener diode is 10V.



Ans: 0 V

156. LED lamp average a life expectancy of:

Ans: 50000 hrs

157. The output resistance (in $k\Omega$) of a common base transistor, circuit is of the order of :


Ans: None of these

158. A transistor has a current gain of 0.99 in common base mode. Its current gain in common emitter mode is

Ans: 99

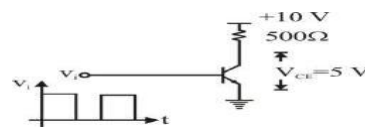
159. The switching transistor as shown, carries in the collector side an rms current of 8 mA. If the

frequency of rectangular pulse train v_i is 50 Hz, then on-time of the transistor is



Ans: 12.8ms

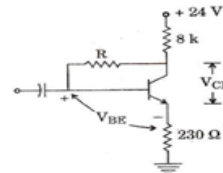160. If the transistor having $V_{CE}=5\text{V}$, $V_{BE}=0.7\text{V}$ has $k\Omega=45$, value of R is



Ans: 85.64k Ω

161. In a CE (Common Emitter) transistor, $V_{CC}=12\text{ V}$ and the zero signal collector current is 1 mA. Determine the operating point when collector load (R_{ANS} : is 6k Ω

Ans: 6 V, 1 mA


162. For a certain transistor, $\beta=50$. Find the value of α .

Ans: 0.98

163. Calculate the value of emitter current for a transistor with $\alpha_{dc} = 0.98$, $I_{CBO} = 5\mu\text{A}$ and $I_B = 95\mu\text{A}$.


Ans: 5 mA

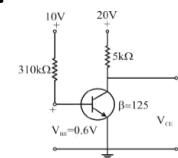164. A transistor is operating in common emitter mode as shown in figure given below. The voltage V_{CE} is.....



Ans: 1.05V

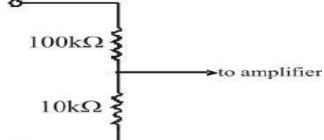165. An attenuator probe as shown, is connected to an amplifier of input capacitance 0.1 μF . Value of C that must be connected across 100k μ to make the overall gain independent of frequency, is




Ans: 0.01 μF

166. A transistor connected in a common base configuration has the following readings: $I_E = 2\text{mA}$ and $I_B = 20\mu\text{A}$, Find the current gain.

Ans: 0.99

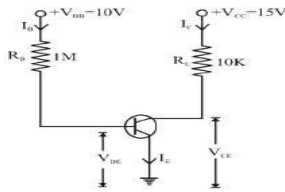167. Find the approximate collector current in the given transistor circuit. (Take current gain, $\beta = 100$)



Ans: 1 mA

168. A delayed full-wave rectified sinusoidal current has an average value equal to one-third is maximum value. Find the delay angle.

Ans: $\cos^{-1} 0.047$


169. 2's complement of the number of 1010101 is

Ans: 0101011

170. In Excess-3 code the 4-bit group that is used is


Ans: 0011

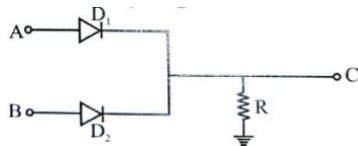171. Which of the following logical operations could be computed by the given network?



Ans: $C = A + B$

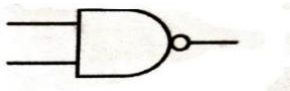172. The standard 2-input TTL gate for the below shown electrical symbol is



Ans: 7400

173. If the range of an analog transducer is 0 to 10V, then for a resolution of 5mV, the bits of ADC will be.....

Ans: 11

174. In Boolean algebra (A.ANS: + A = ?


Ans: A

175. 160 A transistor connected in a common base configuration has the following readings: $I_E = 2\text{mA}$ and $I_B = 20\mu\text{A}$, Find the current gain.

Ans: 0.99

176. Find the approximate collector current in the given transistor circuit.

(Take current gain, $\beta = 100$)

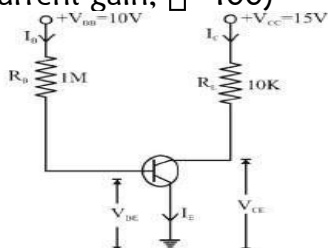

Ans: 1 mA

177. For a CE configuration, the transistor supply voltage is 12V. The load resistance is 900Ω. The voltage drop across load resistance is 0.9V. The value of collector-emitter voltage is _____

Ans: 11.1V

178. The gain of a CE amplifier is highest at

Ans: Mid frequencies


179. The efficiency of the class B amplifiers Approximately?

Ans: 70% to 100%

180. The input impedance of an amplifier is:


Ans: V_{in}/I_{in}

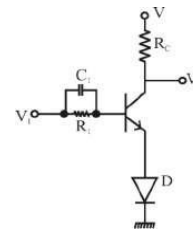181. In the given circuit the function of the diode D is




Ans: To protect the base-emitter junction

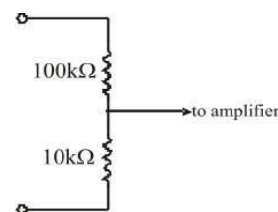182. An attenuator pro beas shown, is connected to an amplifier of input capacitance $0.1\mu\text{F}$. Value of C that must be connected across $100k\Omega$ to make the overall gain independent of frequency, is




Ans: $0.01\mu\text{F}$

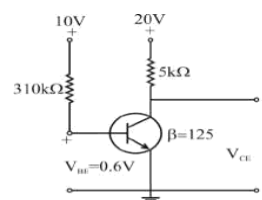183. A transistor is operating in common emitter mode as shown in figure given below. The voltage V_{CE} is.....




Ans: 1.05V

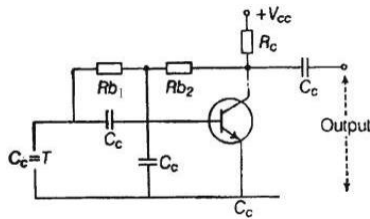184. What is the method of biasing used in the amplifier circuit shown in the figure?




Ans: Collector to base bias

185. Figure represent

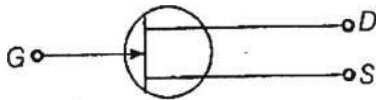

Ans: Junction field effect transistor

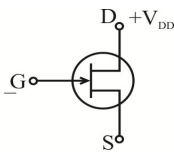186. Identify the device based on the given symbol.



Ans: N-channel JFET

187. Choose the correct statement when $V_{GS} = 0$ and $V_{DS} = 0$ in a JFET.

Ans: The depletion regions around the p-n junctions are equal in thickness and symmetrical

188. The threshold voltage of an n-channel MOSFET can be increased by.....

Ans: Reducing the gate oxide thickness

189. The transit time of the current carriers through the channel of an FET decides its characteristics:

Ans: Switching